

## UPDATE Problem 4: $R_s$ changed!

Midterm Practice (optional, similar problems will be on the midterm). Solutions available in office hours and on bspace 10/17/2012.

### Midterm:


- Open-book, one 8.5 by 11 inch page of handwritten notes (two sided)
- Write all your work and answers on the exam sheet
- Clearly mark results with a box around them
- Show your work (large and small-signal circuit diagrams, design equations)
- ~~Cross out incorrect answers.~~ If you present two or more inconsistent answers we invariably grade the wrong one.
- All problems have equal weight.
- Notation:  $V_x = V_X + v_x$ , where  $V_X$  is the large signal bias and  $v_x$  is the small signal value.
- The math is trivial for all problems on the midterm, if approached correctly. This is not a course about complicated algebra and calculus!

Use the following parameters in all problems, unless otherwise specified:


Device	Parameter values
BJT	$I_s = 1 \text{ fA}$ , $\beta = 100$ , and $V_A = 100 \text{ V}$
NMOS	$ V_{TH}  = 400 \text{ mV}$ , $\mu_n C_{ox} = 200 \mu\text{A}/\text{V}^2$ , $\lambda = 0.02 \text{ V}^{-1}$ , $\gamma = 0 \text{ V}$ .
PMOS	$ V_{TH}  = 400 \text{ mV}$ , $\mu_p C_{ox} = 100 \mu\text{A}/\text{V}^2$ , $\lambda = 0.02 \text{ V}^{-1}$ , $\gamma = 0 \text{ V}$ .

Unless otherwise specified, assume room temperature and  $V_t = 25 \text{ mV}$ .

 
1. The circuit below shows a proposed small-signal model for an MOS transistor biased in the linear (triode) region. Determine all component values from the large signal parameters ( $I_D$ ,  $V_{DS}$ , ...) and transistor characteristics.



2. MOS transistors can be (and often are!) used as resistors. Determine  $W$  such that the large-signal channel resistance  $R_{DS} = |V_{DS}/I_D| = 10 \text{ k}\Omega$  for  $V_{DS} = 1 \text{ V}$  and  $V_{GS} = 3 \text{ V}$ . What is the value of the small-signal channel resistance  $r_{ds} = |v_{ds}/i_d|$ ?

 

 3. Calculate the small-signal voltage gain  $a_v = v_o/v_s$  and small-signal output resistance at port  $V_o$  of the circuit below.



4. Design a circuit such that  $a_v = v_o/v_s = 1$  ( $\pm 2\%$ ) using a single NPN transistor and as many resistors and (ideal) bias sources (current or voltage) as you like (fewer is better and helps avoid mistakes). The value of  $R_s$  varies in the range  $1 \dots 6k\Omega$  and  $R_L = 5k\Omega$ . Stay close to the minimum power dissipation (not more than  $2x$ ).

Use the following sequence (you may need to iterate):

- Determine the type of amplifier configuration (CE, CB, CC) best suited for this problem.
- Draw a prototype large signal model including all biasing elements. You may need to iterate, e.g. modify or add biasing elements during the design process.
- Draw the small-signal diagram and determine the small-signal parameters required to meet the specifications.
- Calculate the large signal parameters including the values of all bias sources.
- Verify that your circuit meets the specifications.

