

# EE 105

## Microelectronic Devices and Circuits

Bernhard E. Boser

University of California, Berkeley

[boser@eecs.berkeley.edu](mailto:boser@eecs.berkeley.edu)


Copyright © 2012 by Bernhard Boser

# Outline

---

- BJT Small-signal model – “second-order effects”
  - Finite Early Voltage,  $V_A$
  - Finite current gain,  $\beta$
  - Other ... finite  $r_b$ ,  $r_e$ , ..., device capacitance (later)
- Biasing
  - Why constant voltage bias won't work
  - Biasing with feedback
  - Biasing with resistors
  - Replica bias circuit
  - Emitter degeneration


# $\mu$ Phone Amplifier

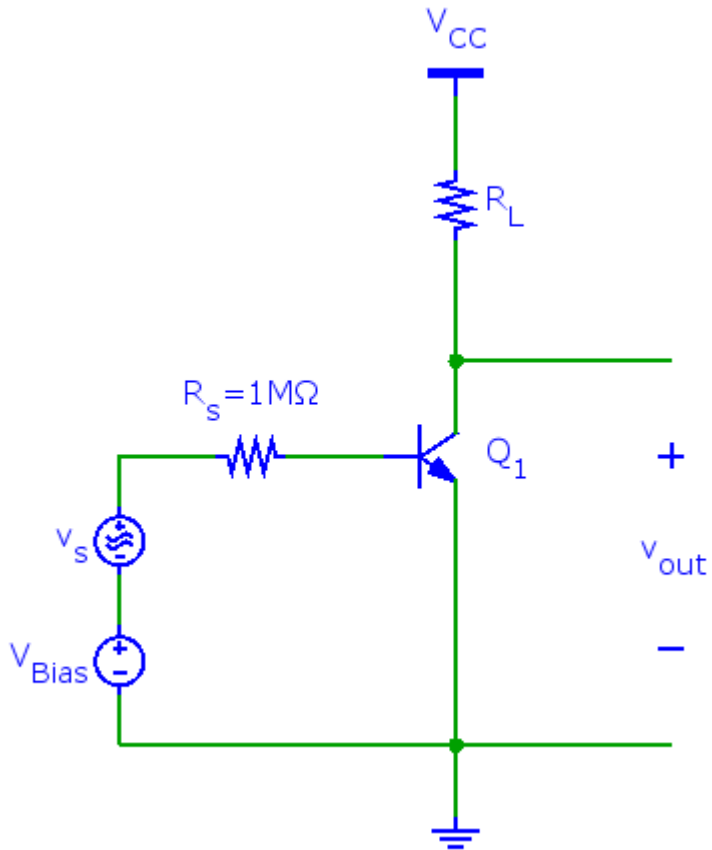

# Finite Current Gain $\beta$


---

# Maximum Gain

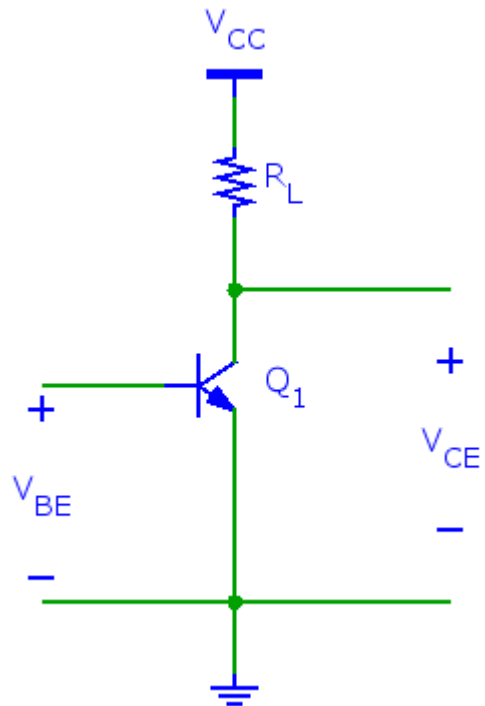

# Current Source “Load”

---

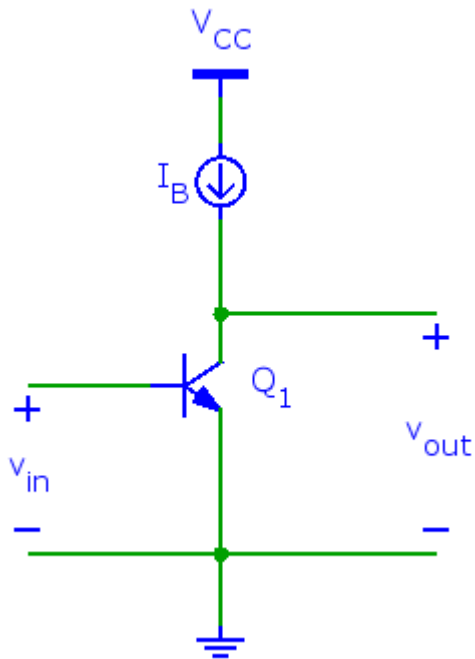

# Early Voltage

---


# ***“Enhanced”* (?!) BJT Small-Signal Model**

---



# Common Emitter with Current Source Load

---

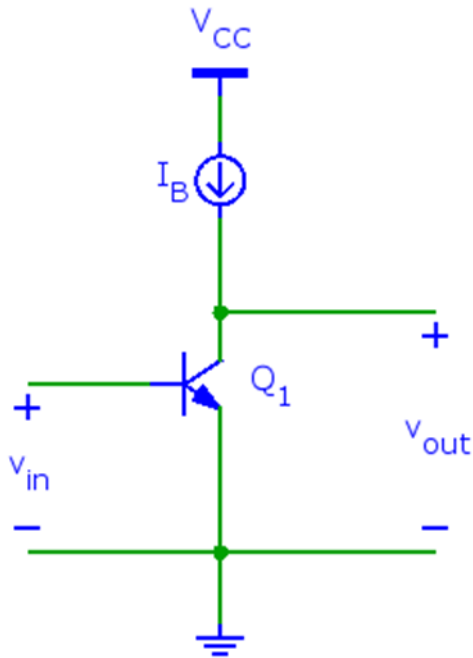


# Transistor Current Source

---

# Active Current Source Bias Options

---

# High-Gain Common-Emitter Amplifier

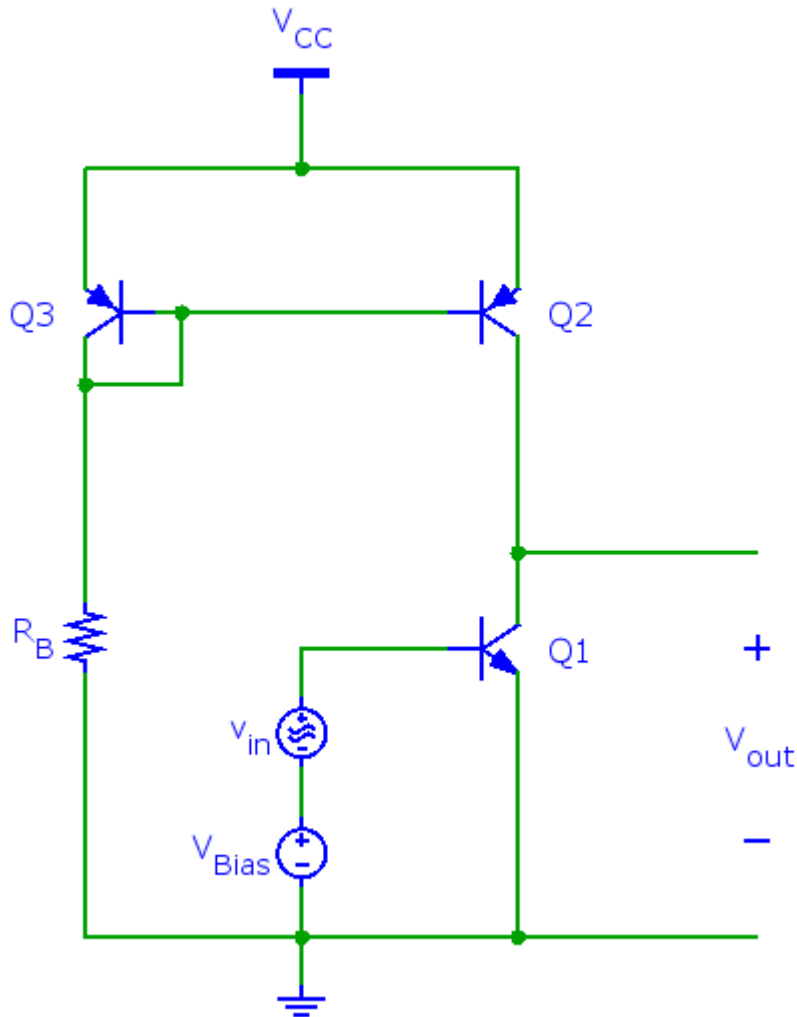


# Small-Signal Summary

---

- Small-signal model
- Linearized about “bias point”
- Parameters are derivative of large signal model
- BJT small-signal model:
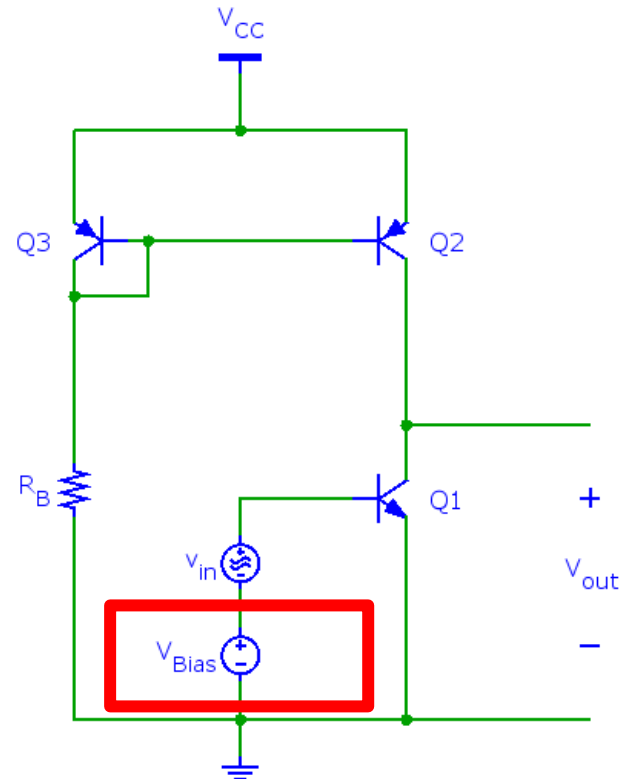
# Biassing


- ~~Constant Voltage~~
- Feedback
- Resistor Bias
- Emitter Degeneration
- Replica Bias



# Bias with Feedback

---


A familiar problem ...

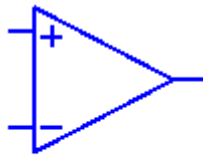

$a_v \rightarrow \text{large}$


**EE 140 covers feedback  
in analog circuits in detail**

# Resistor Biasing

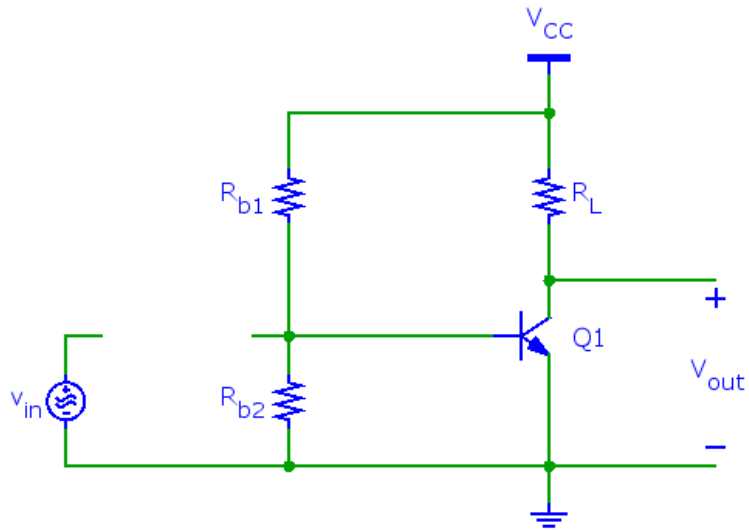




# Resistor Biasing

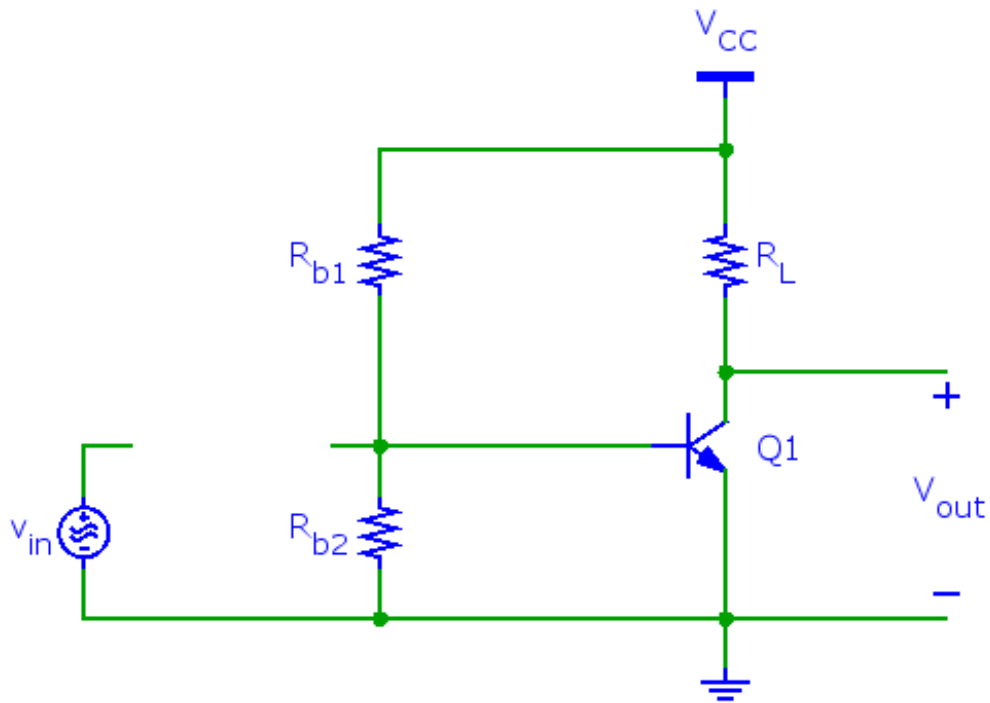

# Emitter Degeneration

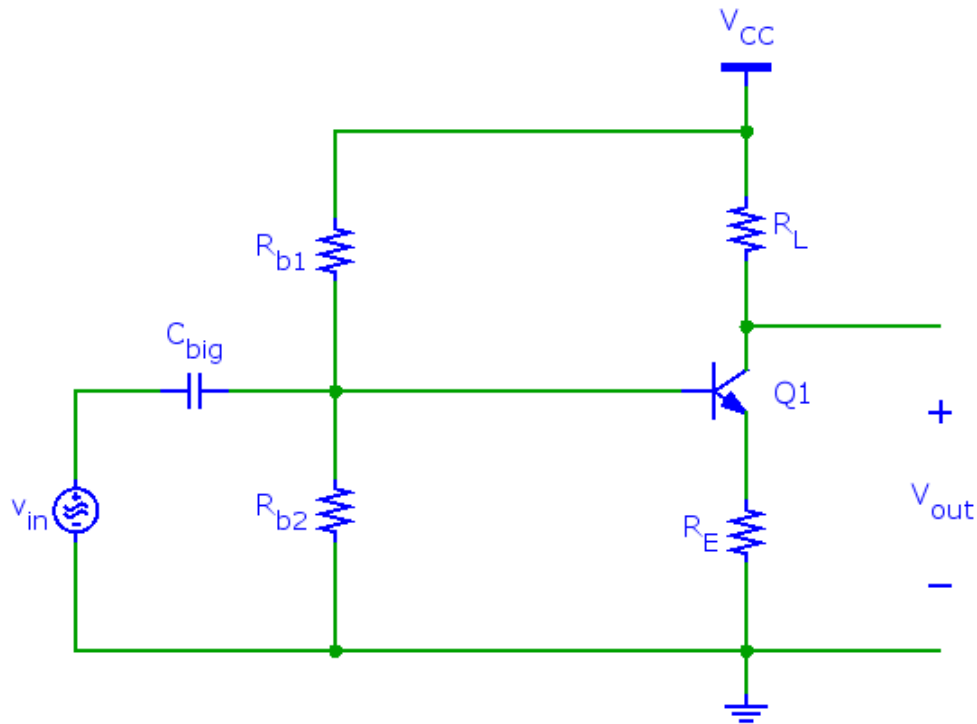

# Outline

---

- BJT Small-signal model – “second-order effects”
  - Finite Early Voltage,  $V_A$
  - Finite current gain,  $\beta$
  - Other ... finite  $r_b$ ,  $r_e$ , ..., device capacitance (later)
- Biasing
  - Why constant voltage bias won't work
  - Biasing with feedback
  - Biasing with resistors
  - Replica bias circuit
  - Emitter degeneration
- Practice!