

Power Transfer Over a **Capacitive** Interface

A Wireless Power Technology

Mitchell Kline

Igor Izyumin

Prof. Bernhard Boser

Prof. Seth Sanders


Why Wireless Power?



Wireless Power Technology


Close-coupled wireless power transfer

Power Source))) Load

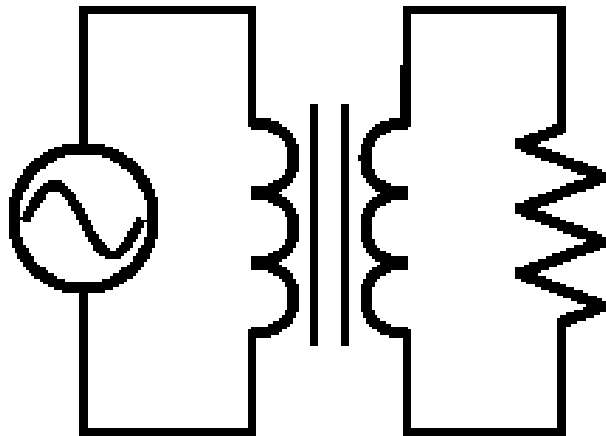


1. Inductive

Power Source))) Load

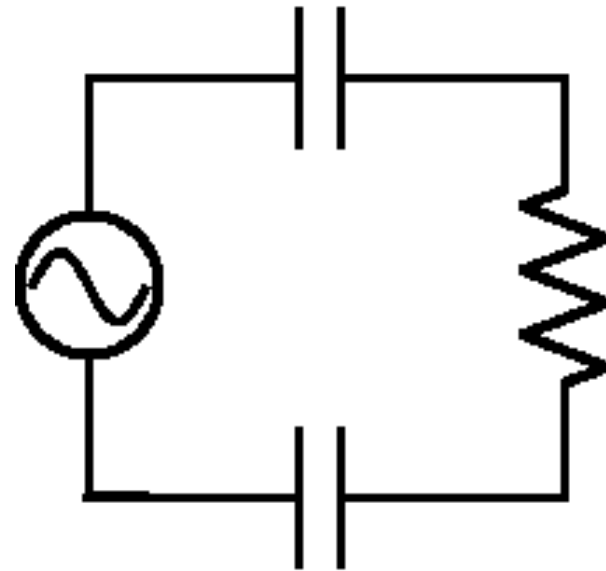

2. Capacitive

The Powermat

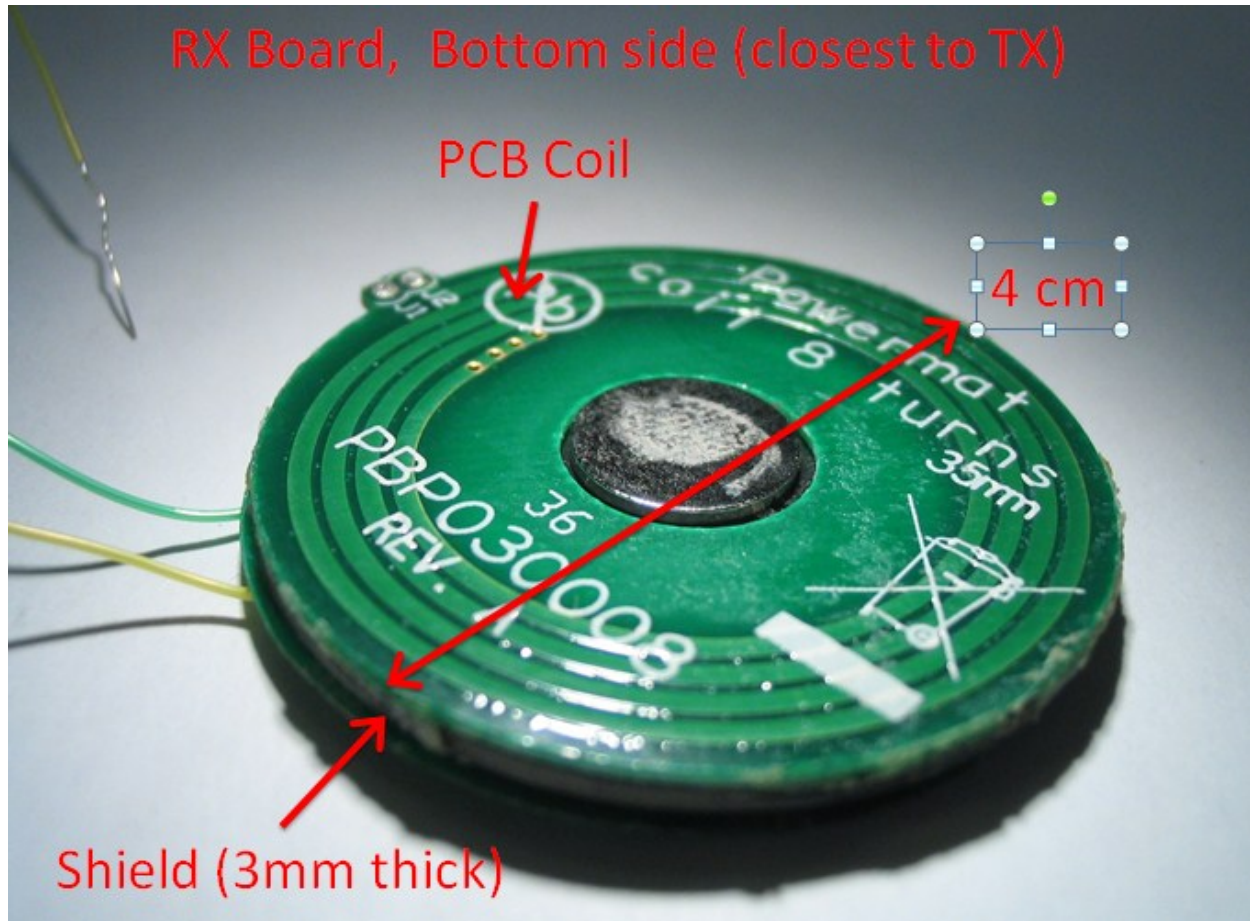

- 60% efficiency
- shield
- up to 1cm gap




Capacitive Charger

Demonstration

Capacitive Power Transfer


Simple
Inexpensive
Thin

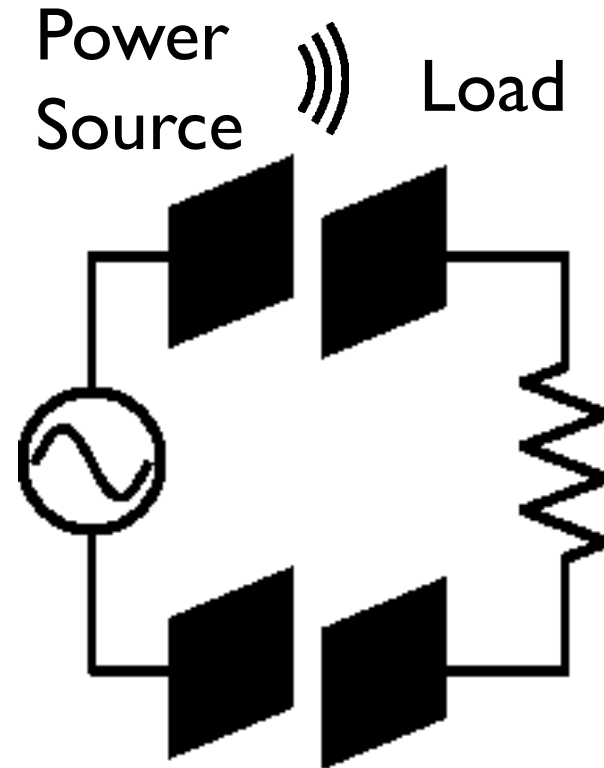

What We Want

1

Small

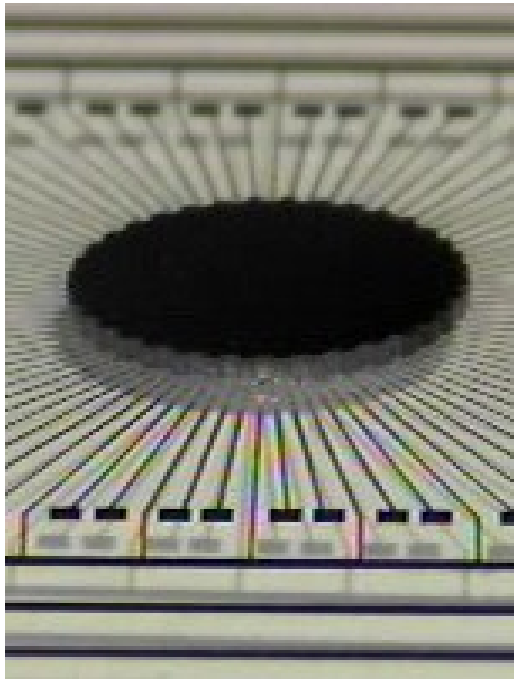


2


Efficient




3

Robust

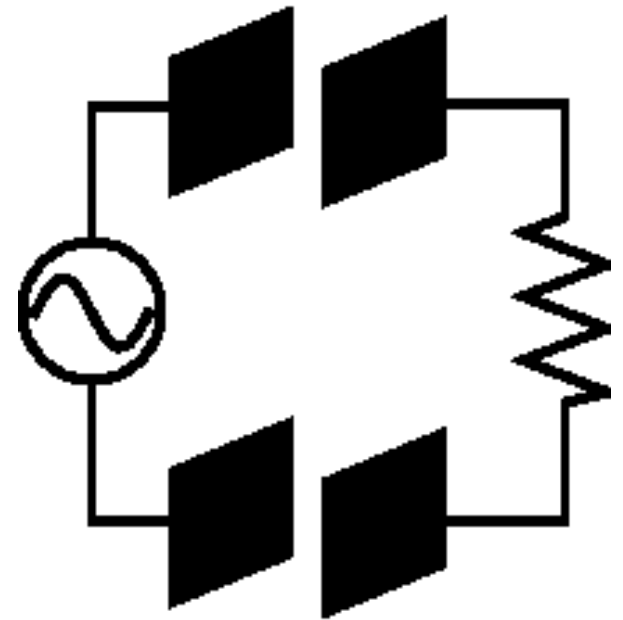


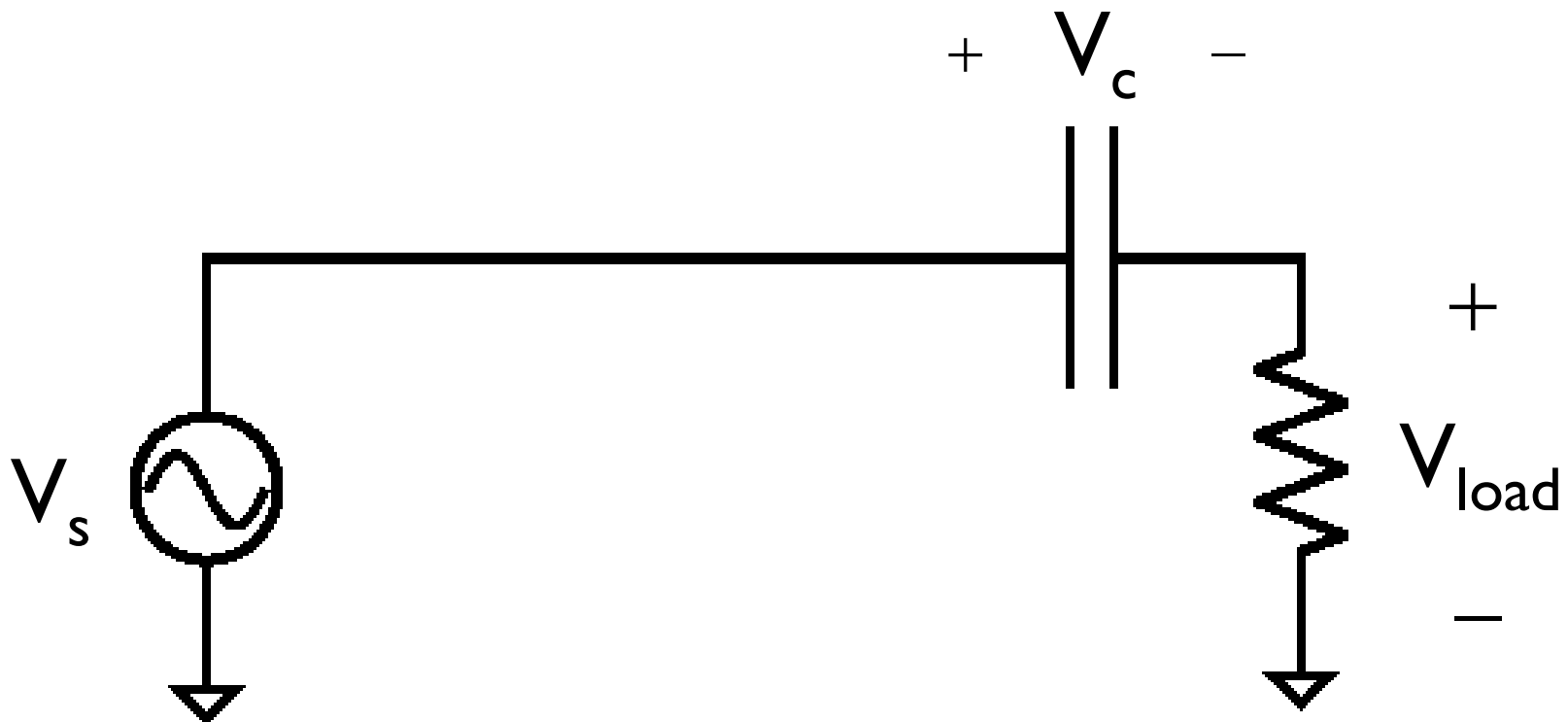

Large capacitor drops little voltage

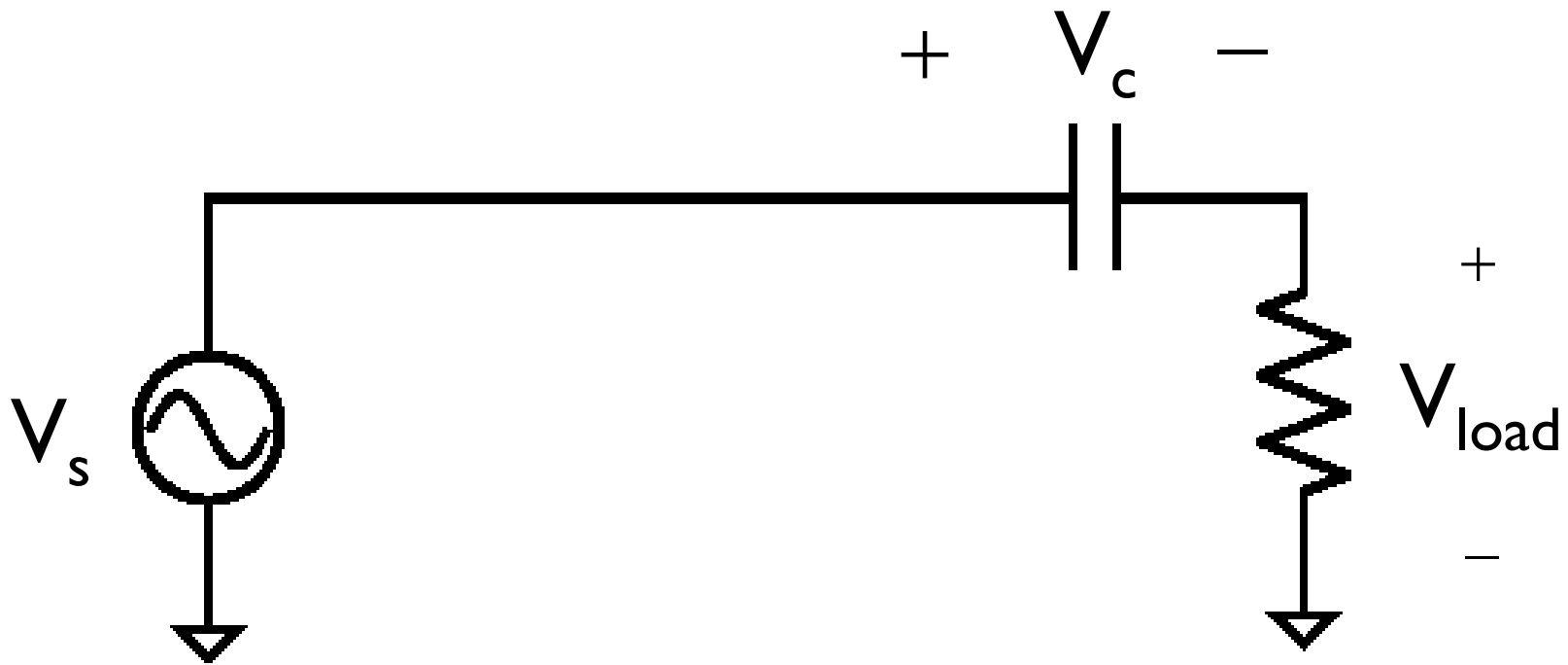

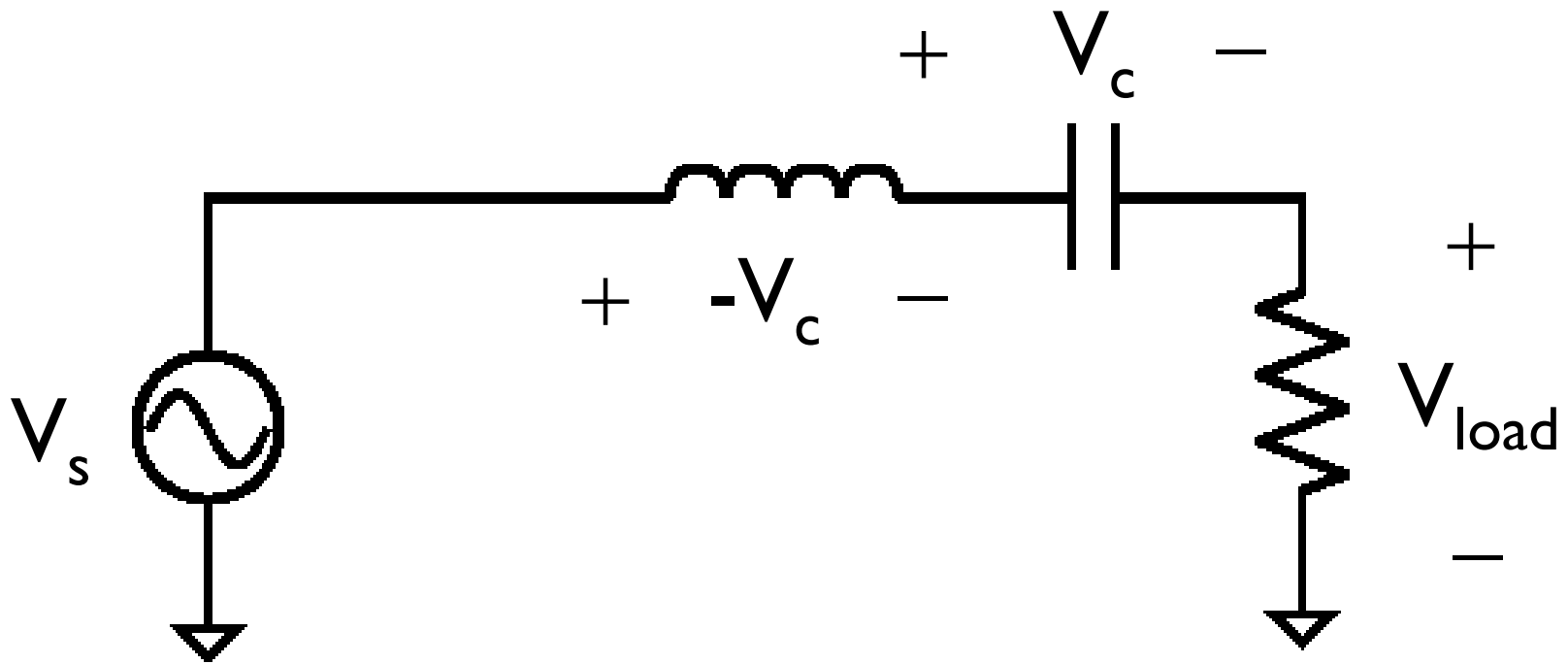Small capacitor drops significant voltage



Inductor compensates for voltage drop




Equivalent circuit at **resonance**

What we want

1

Small

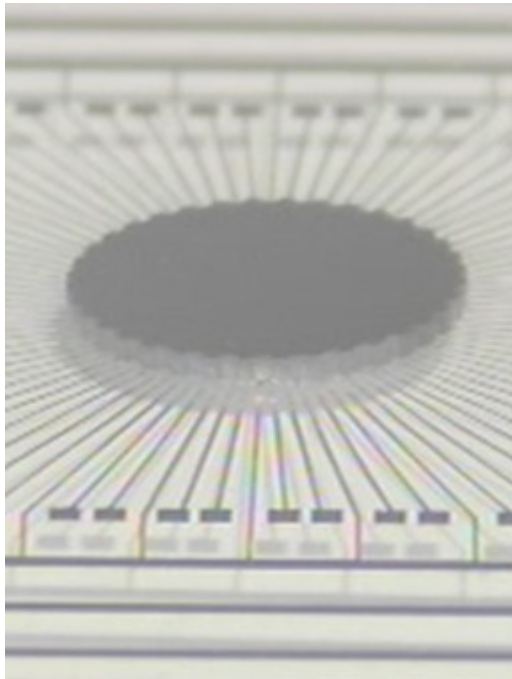


2


Efficient




3

Robust

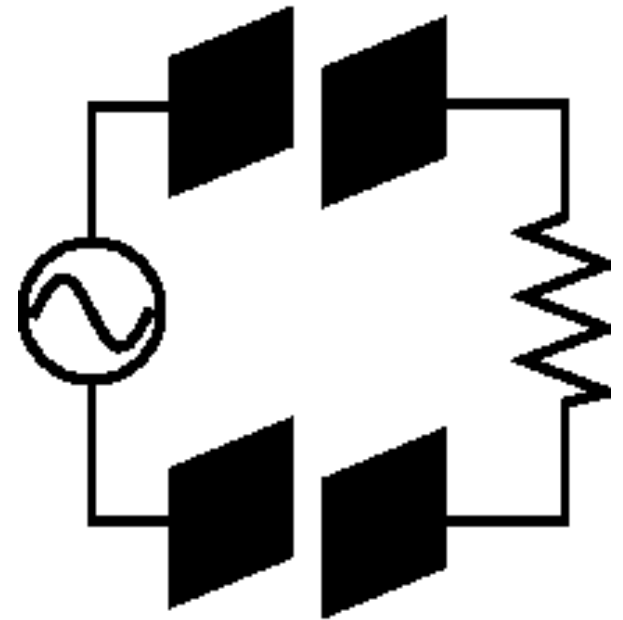


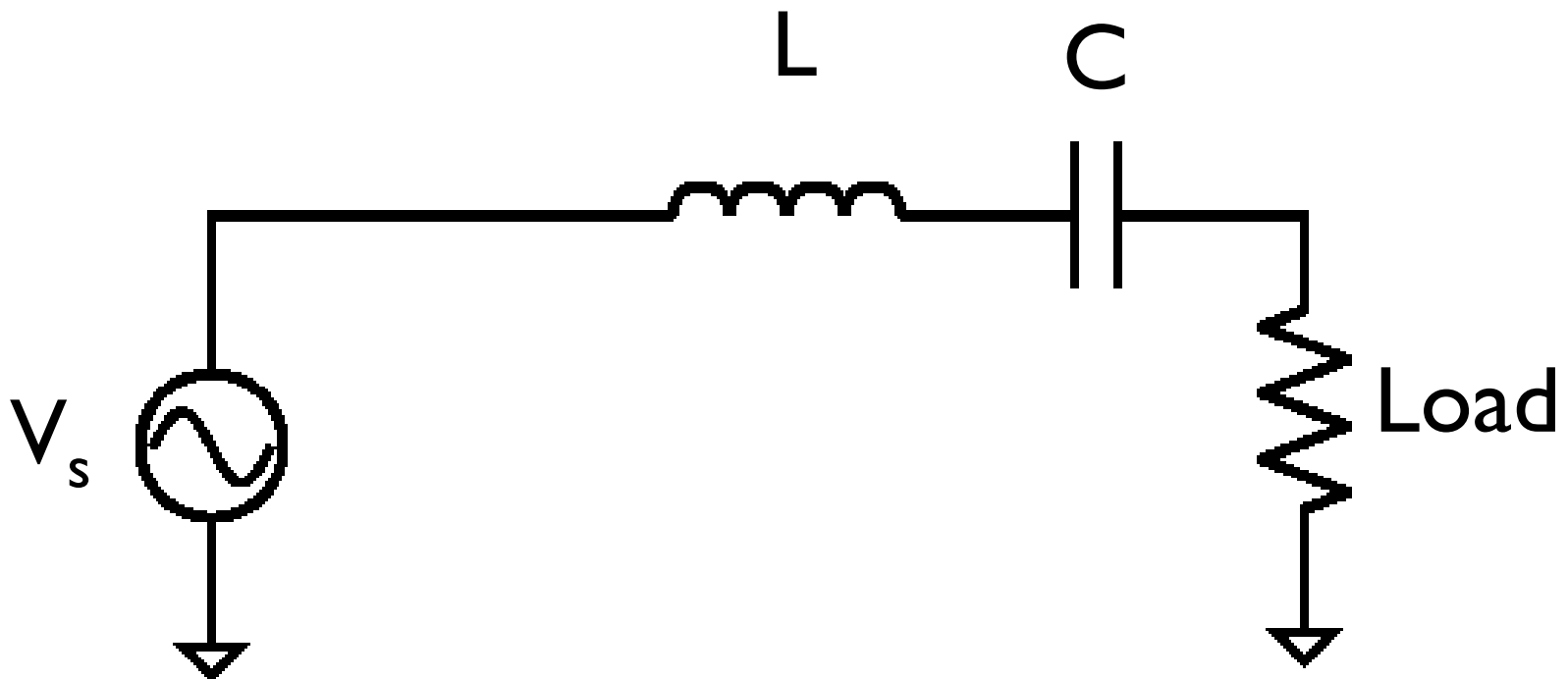


Start with the resonant circuit

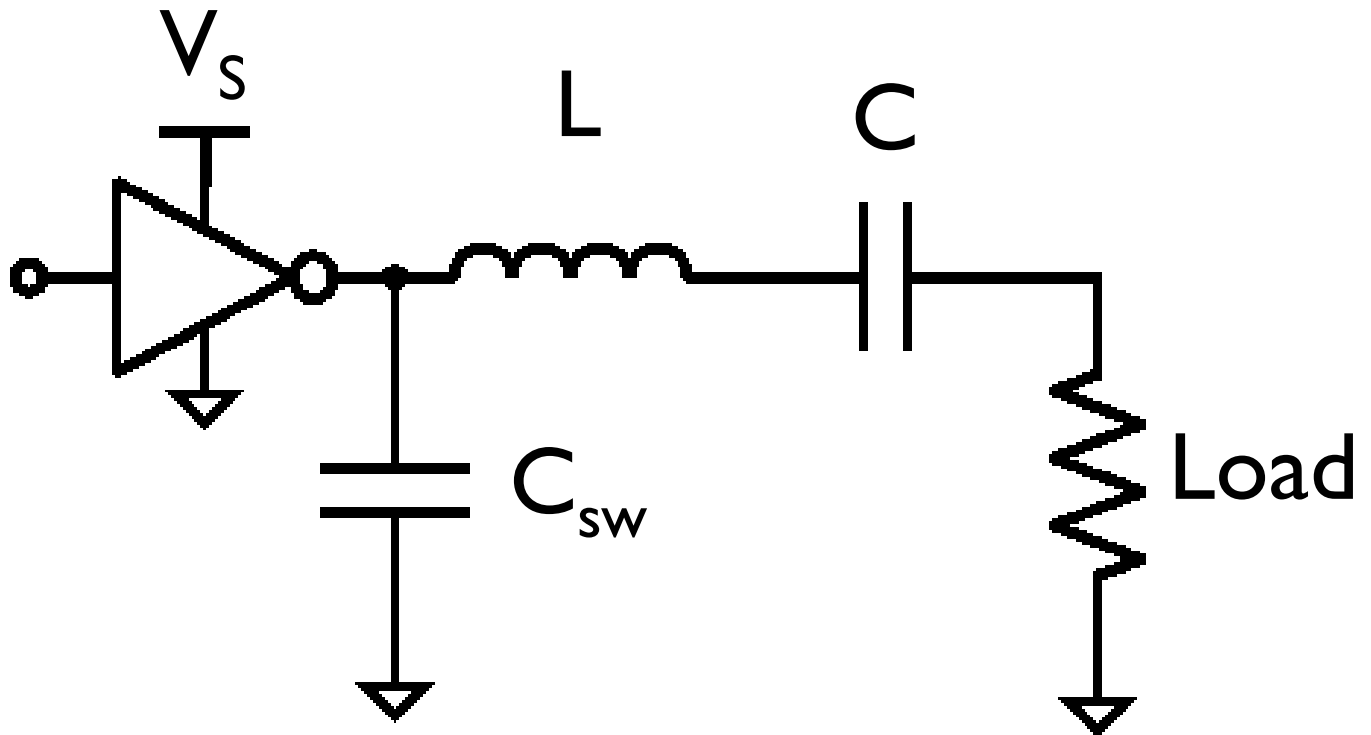


Drive it with an **inverter**

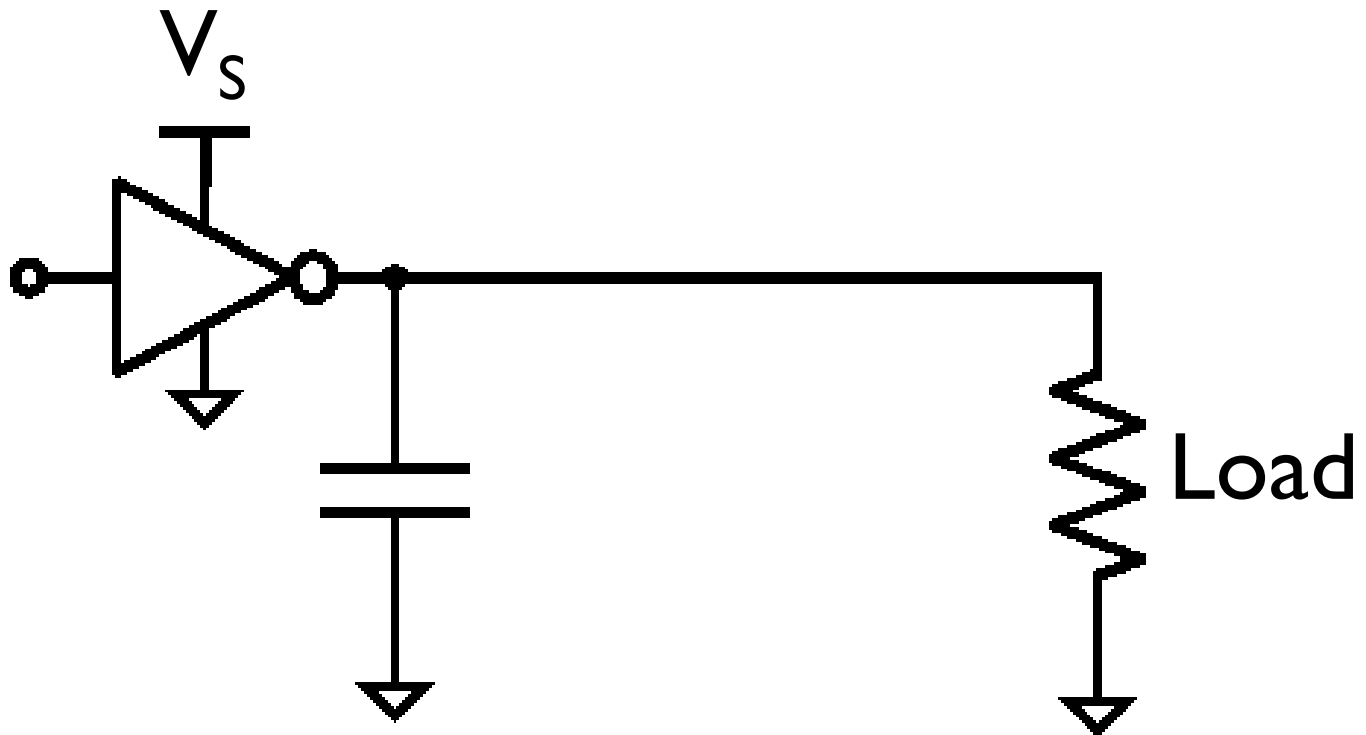

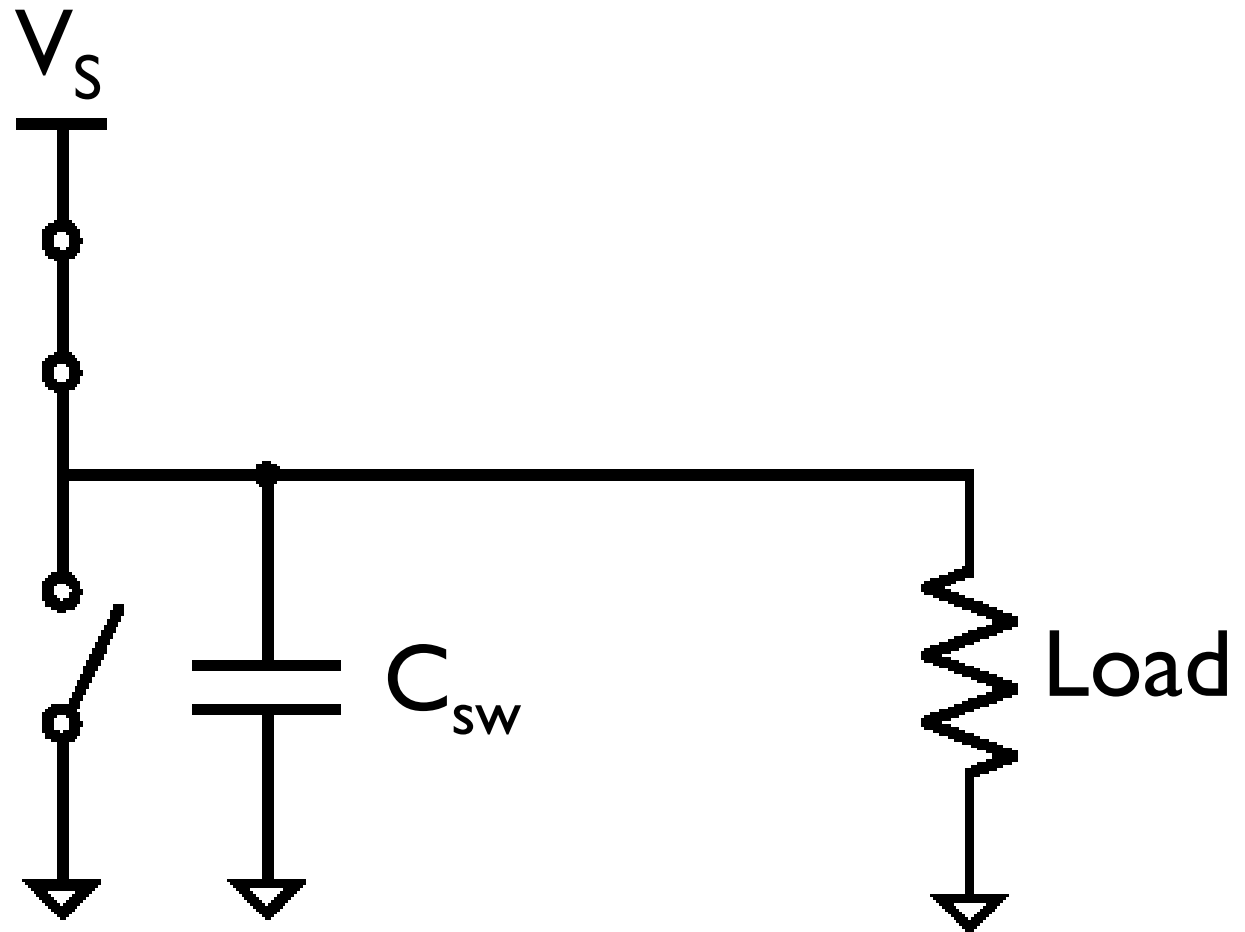
At **resonance**, the output capacitance remains




Turn on the **top** switch

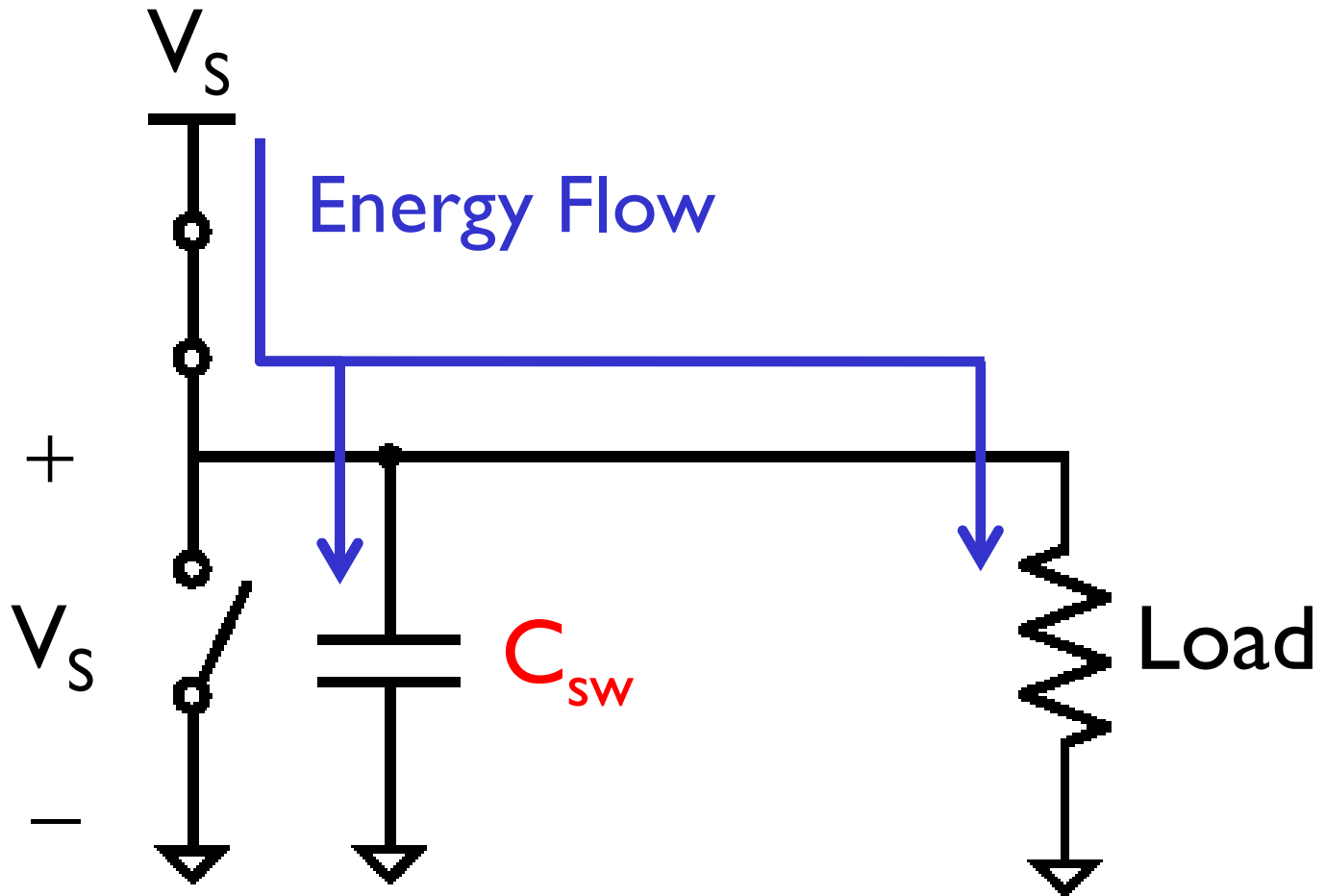


Output capacitor **charged** to V_S

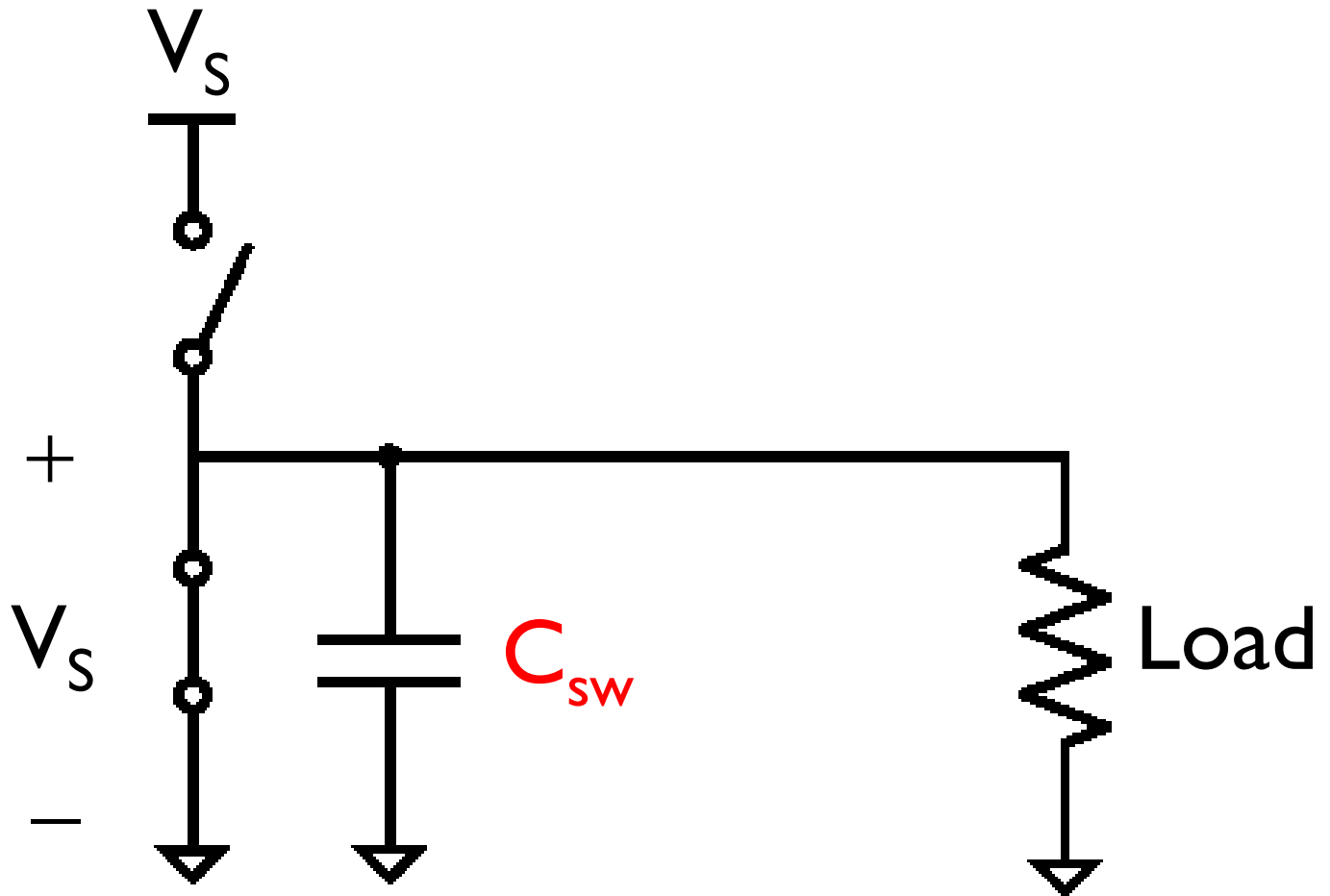


Turn on the bottom switch

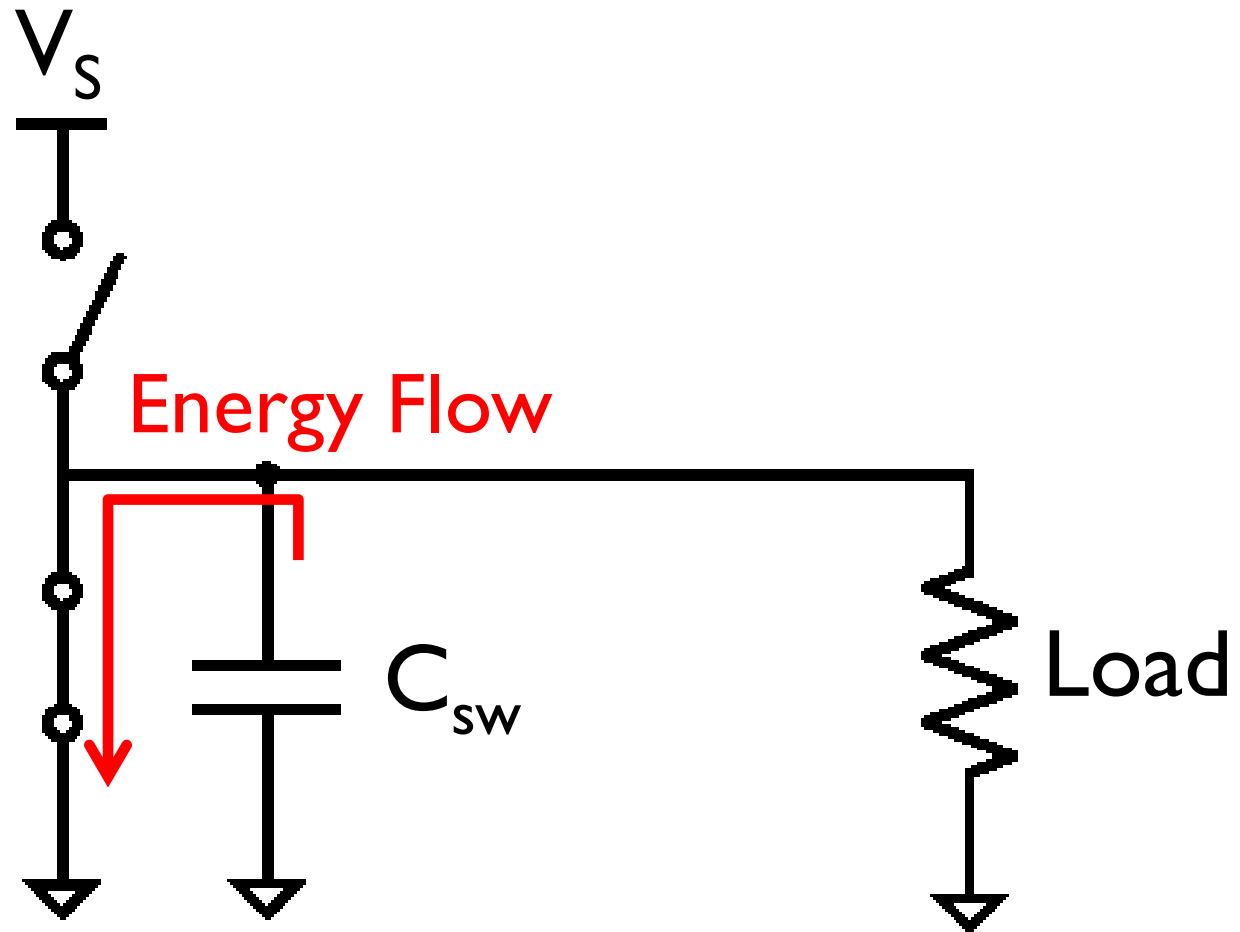


Energy stored on capacitor is **wasted**

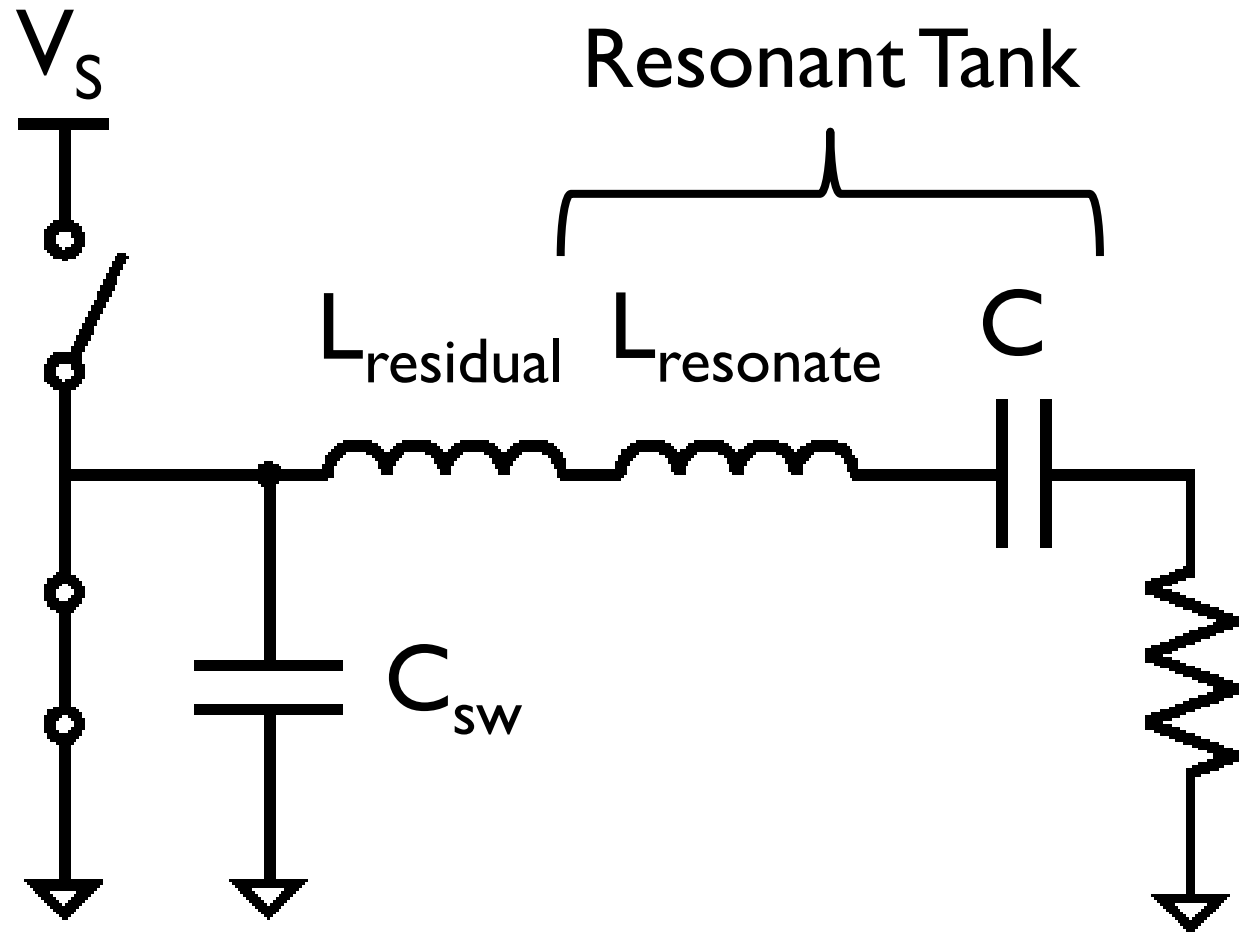


Operate **above** resonance

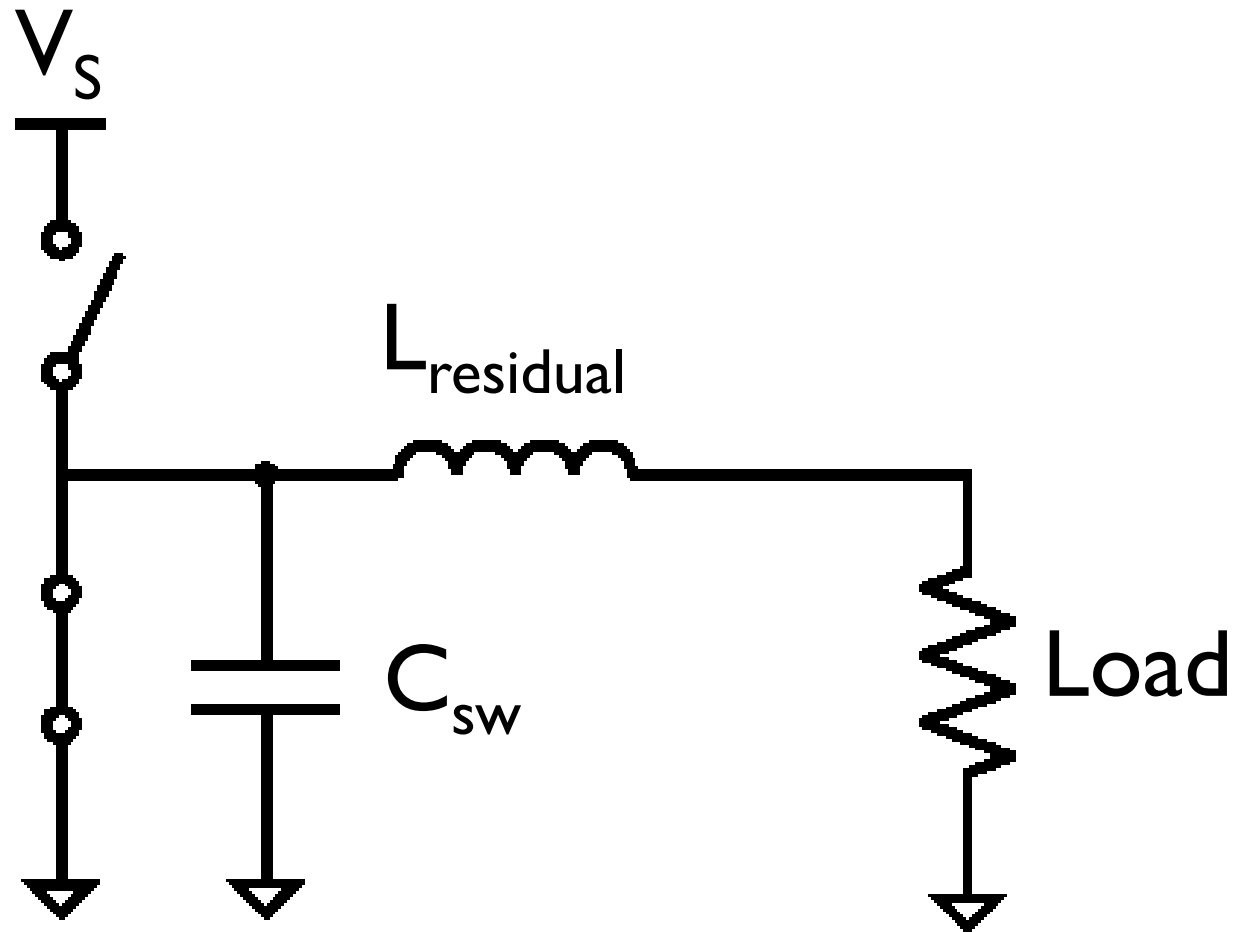


Equivalent circuit **above resonance**

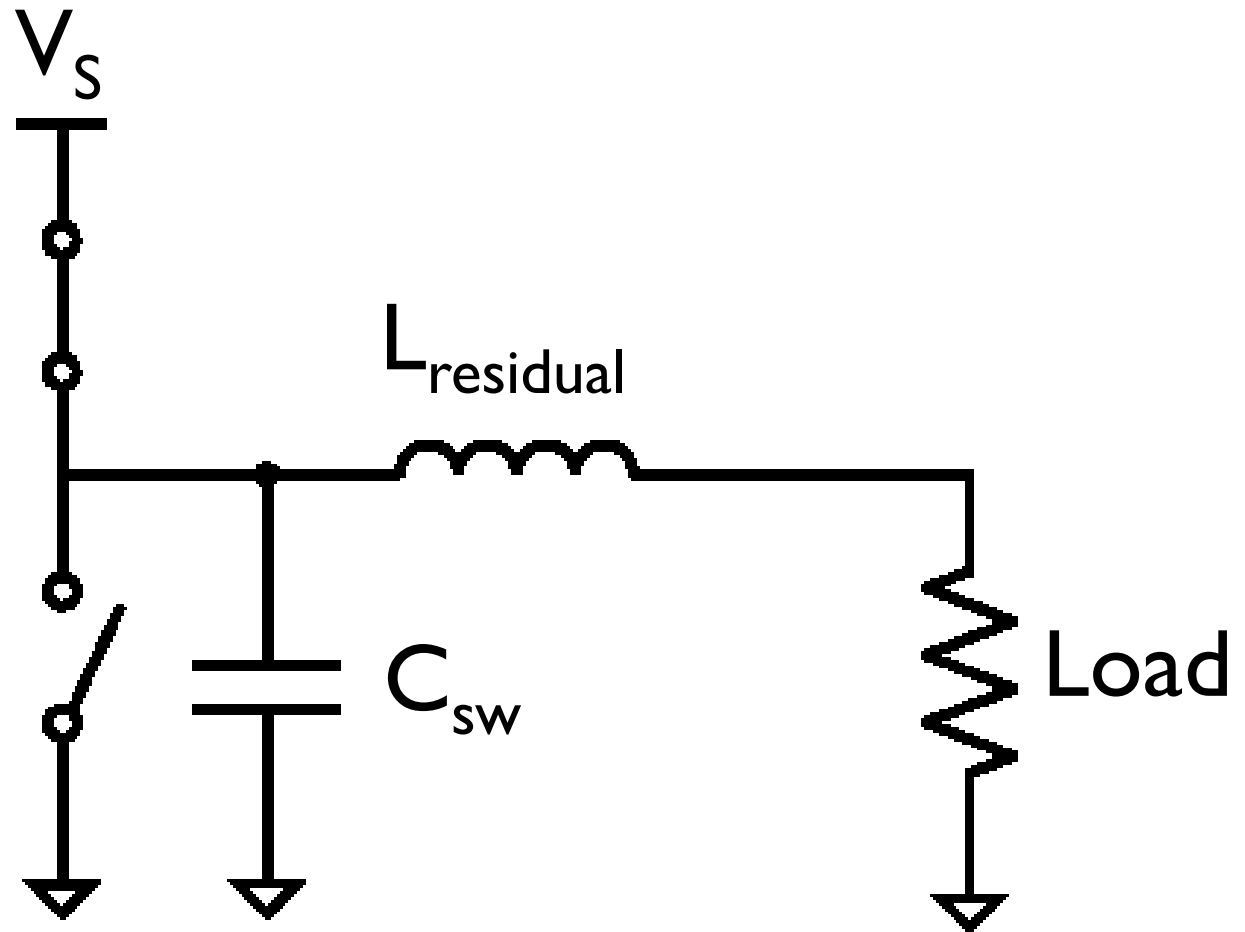


Turn on the **top** switch

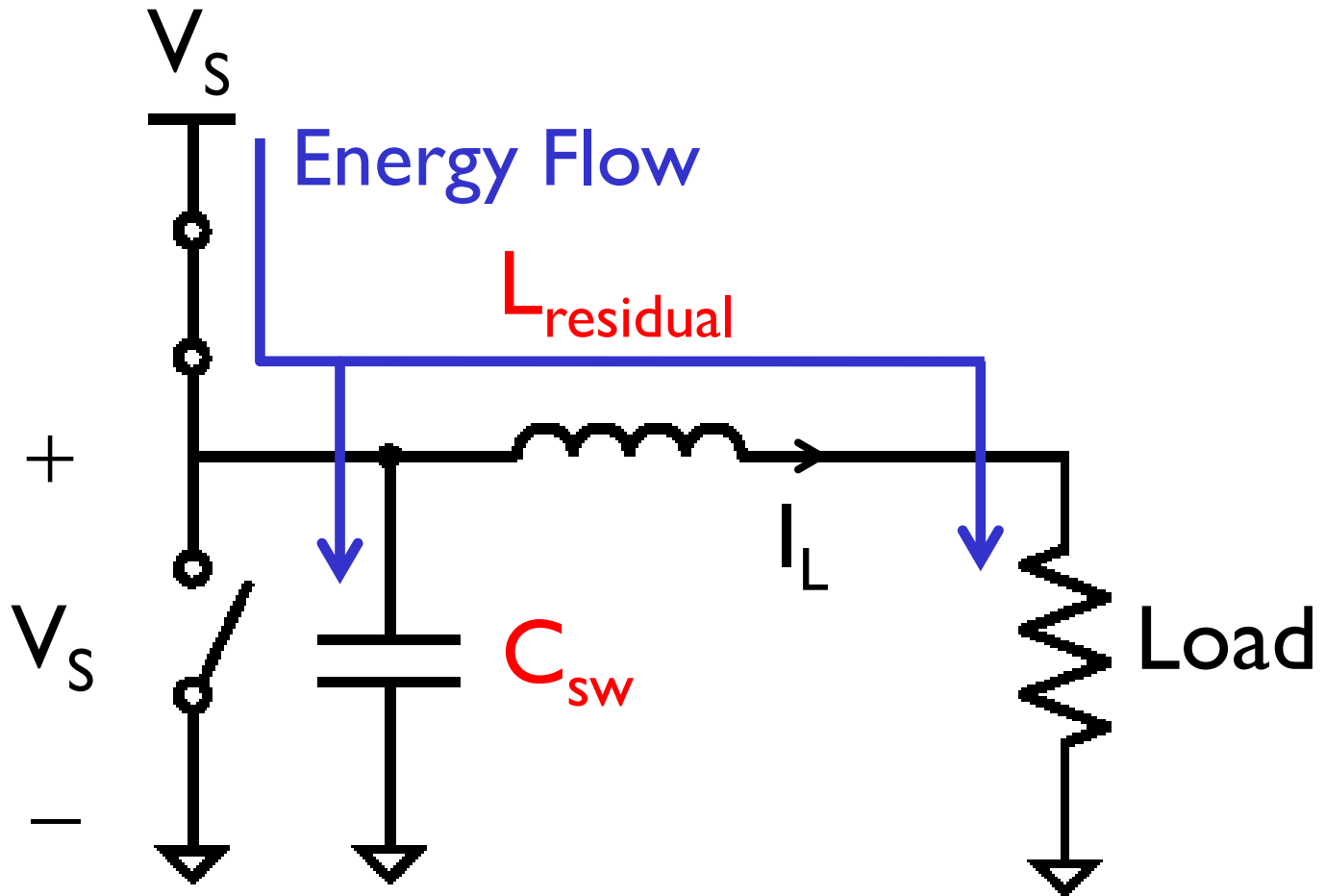

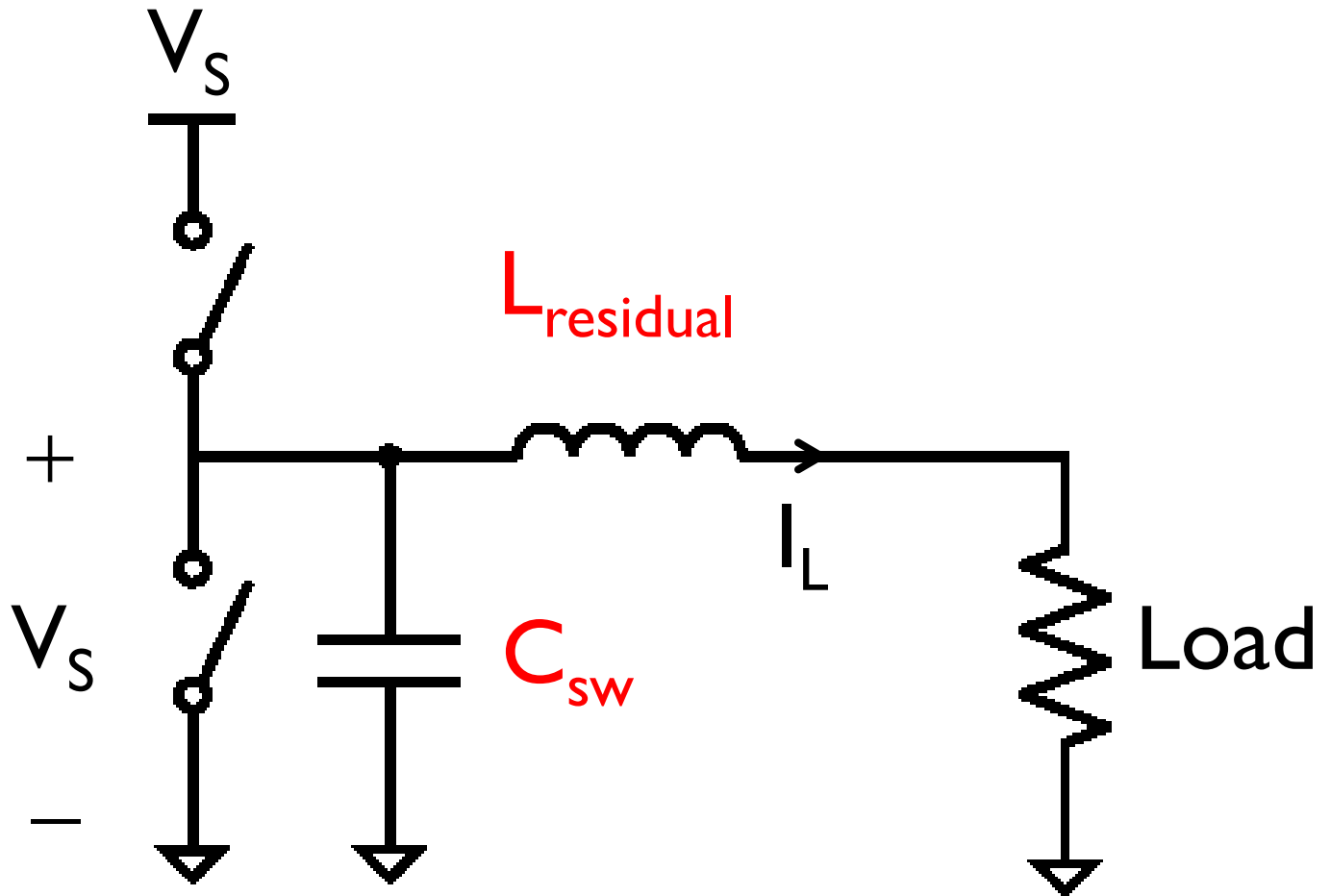
Energy Stored: $\frac{1}{2} C_{sw} V_S^2$ & $\frac{1}{2} L_{residual} I_L^2$




Open both switches

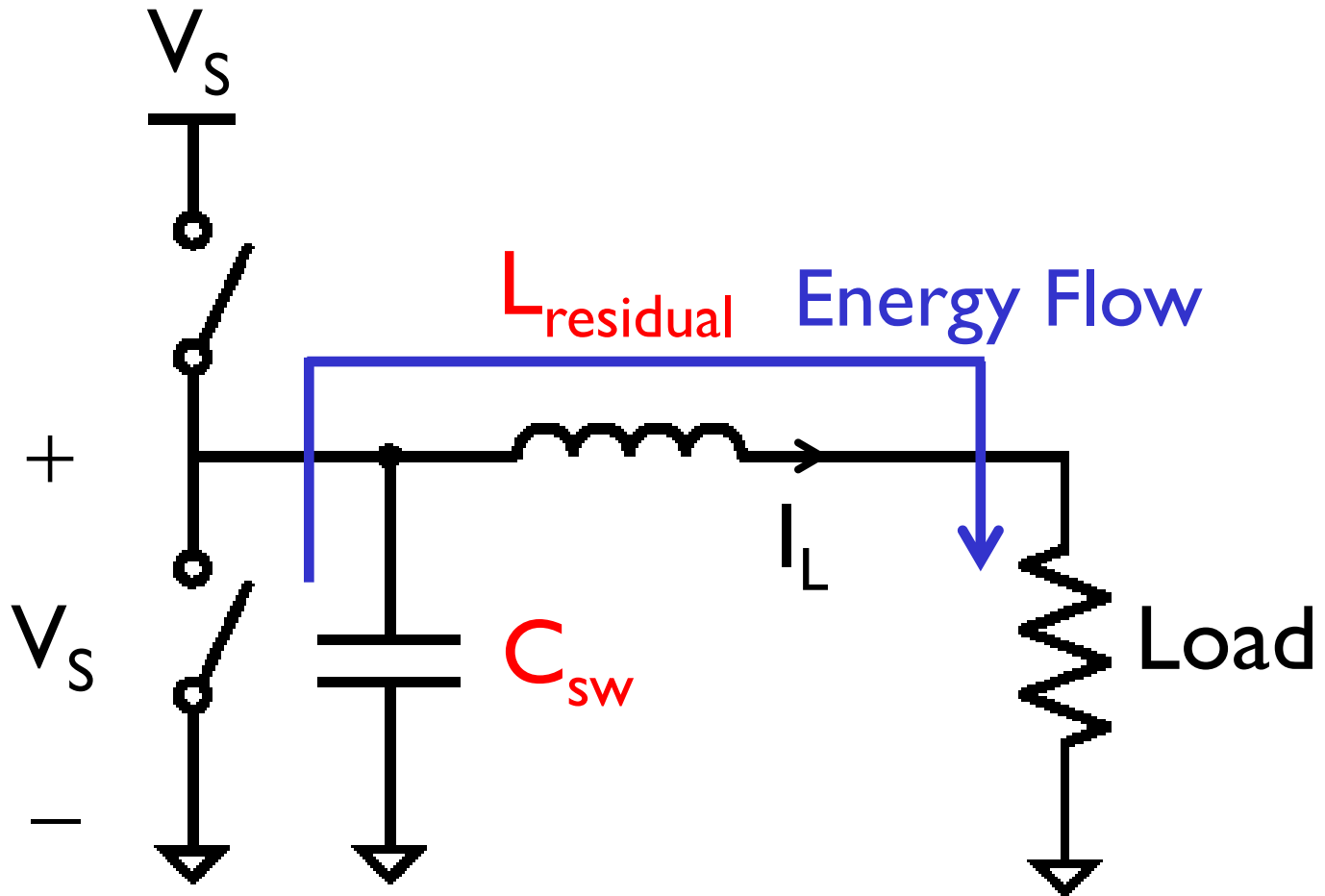

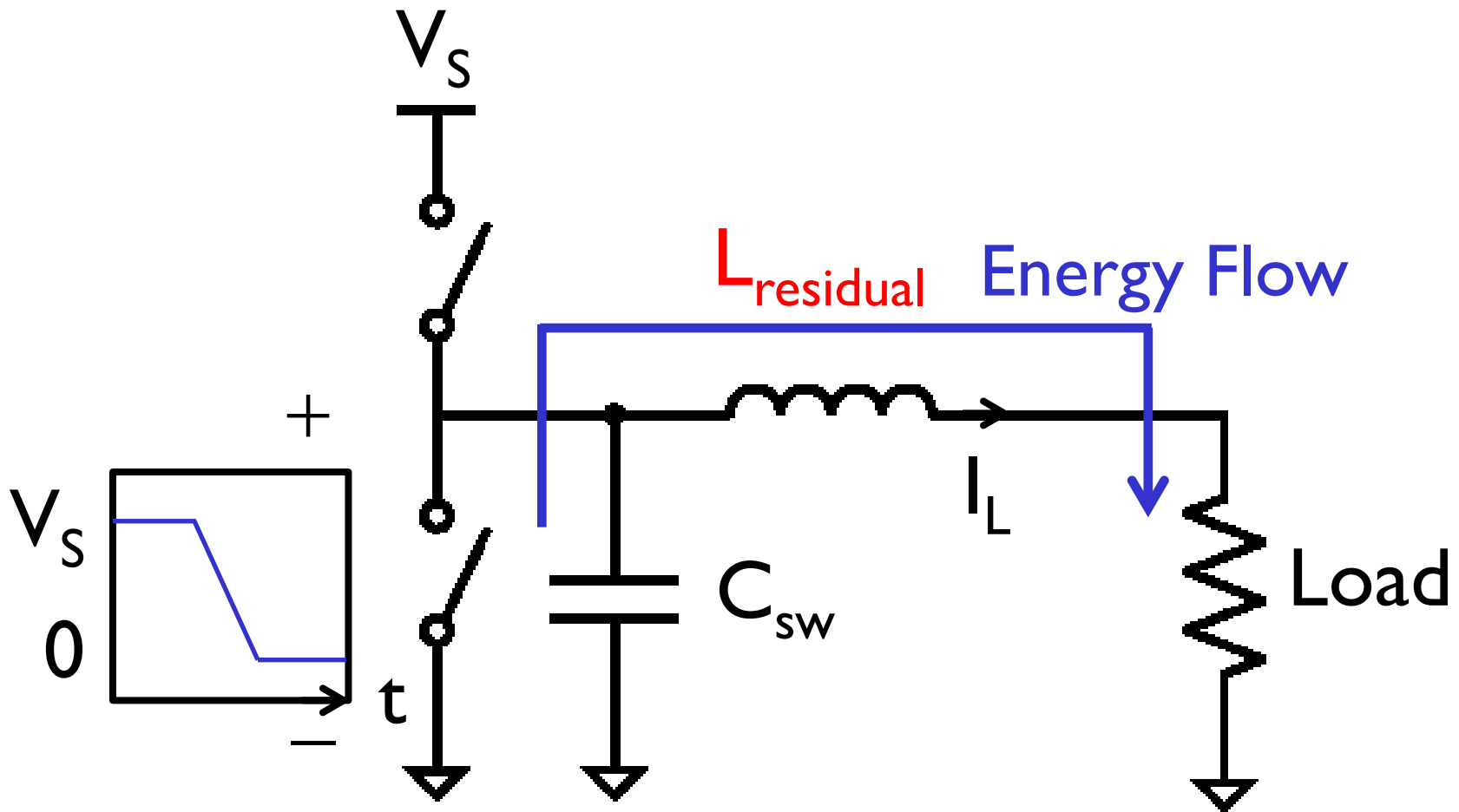
Inductor transfers capacitor energy to load



Output voltage pulled to zero

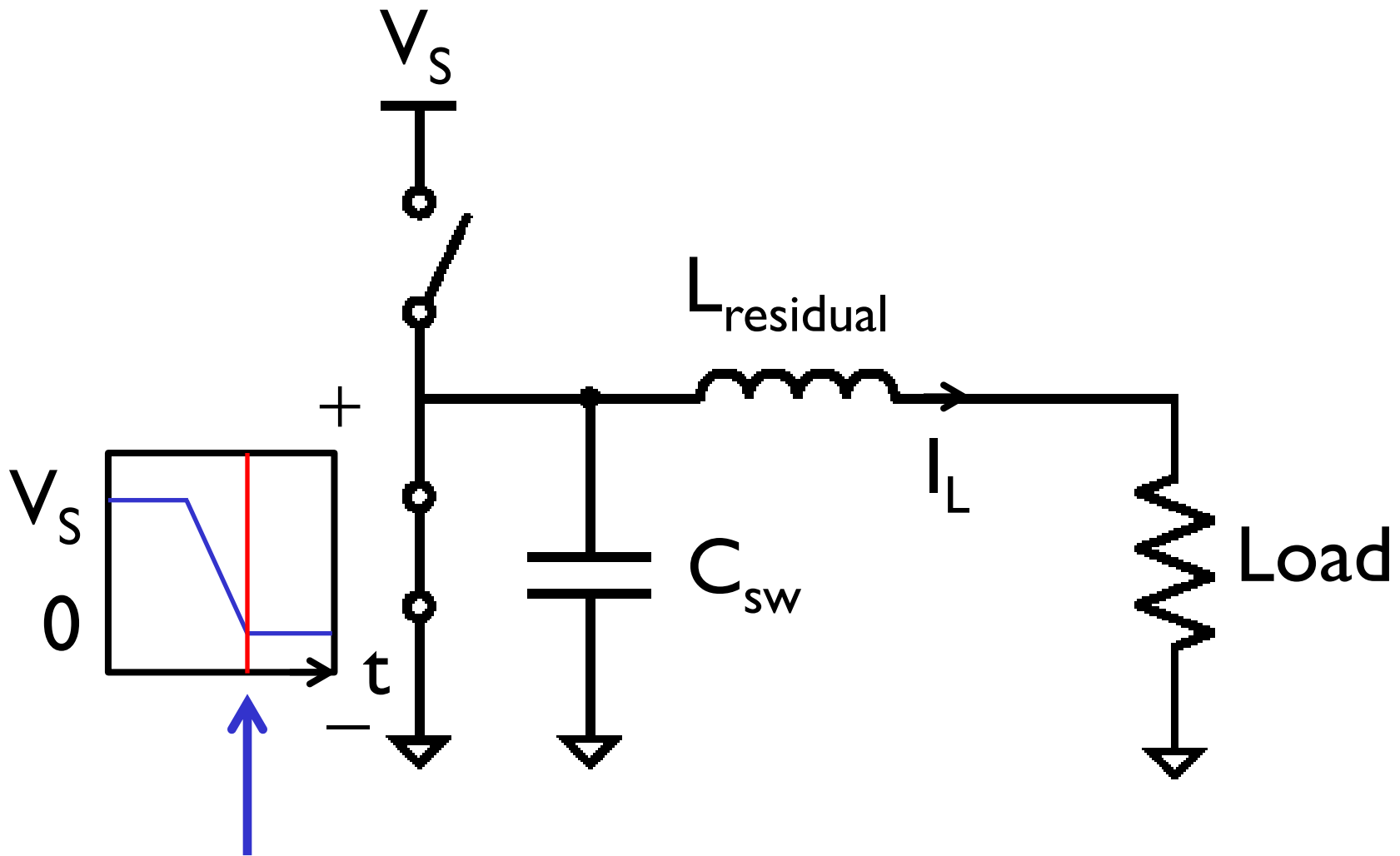

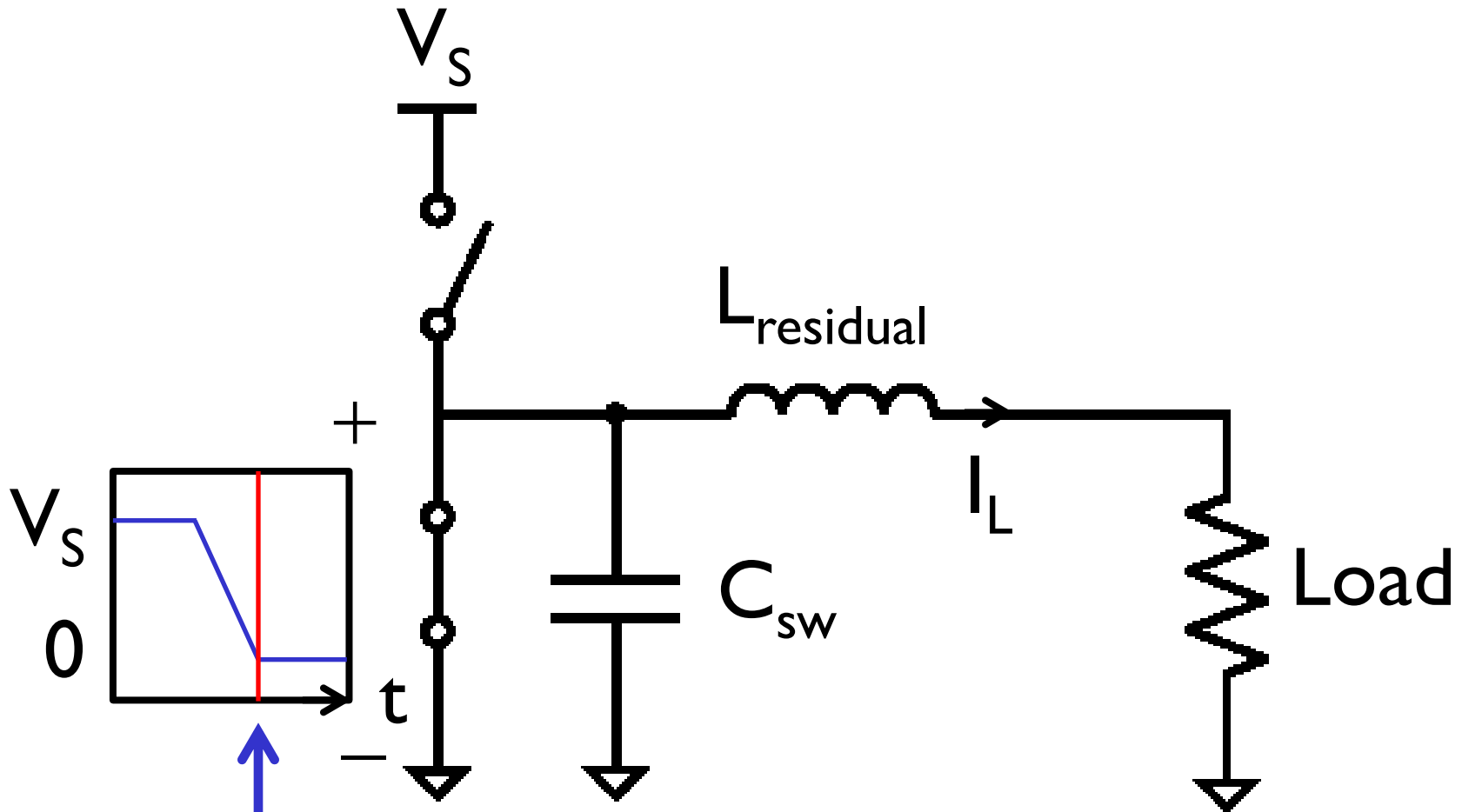Close the switch when the voltage reaches zero




Known as **Zero Voltage Switching (ZVS)**

What We Want

1

Small

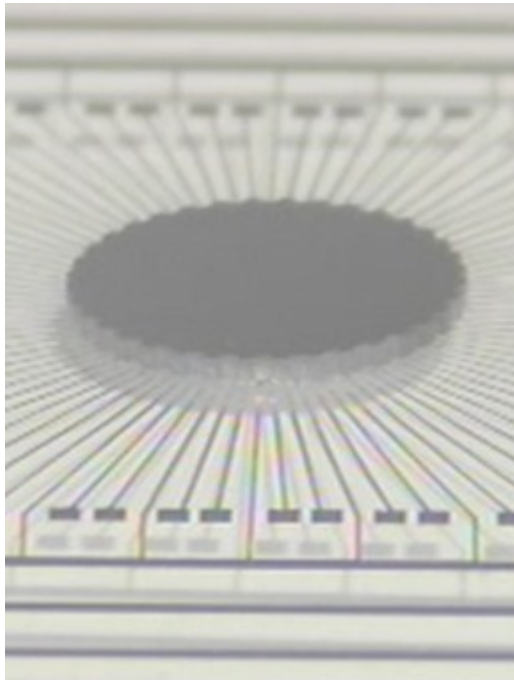


2


Efficient




3

Robust

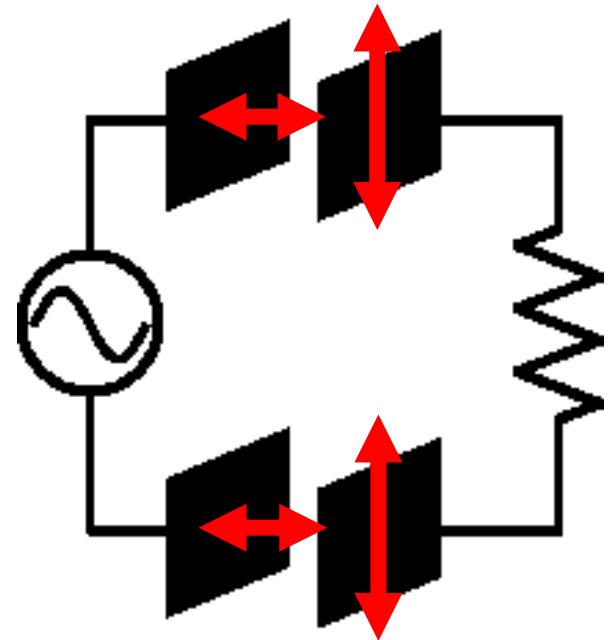

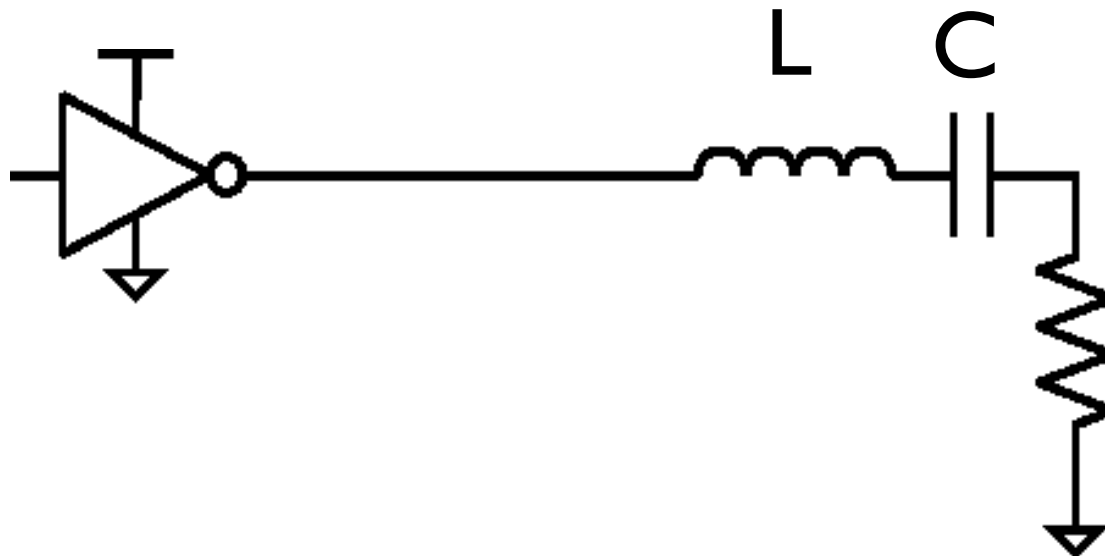


Start with the resonant circuit (again)

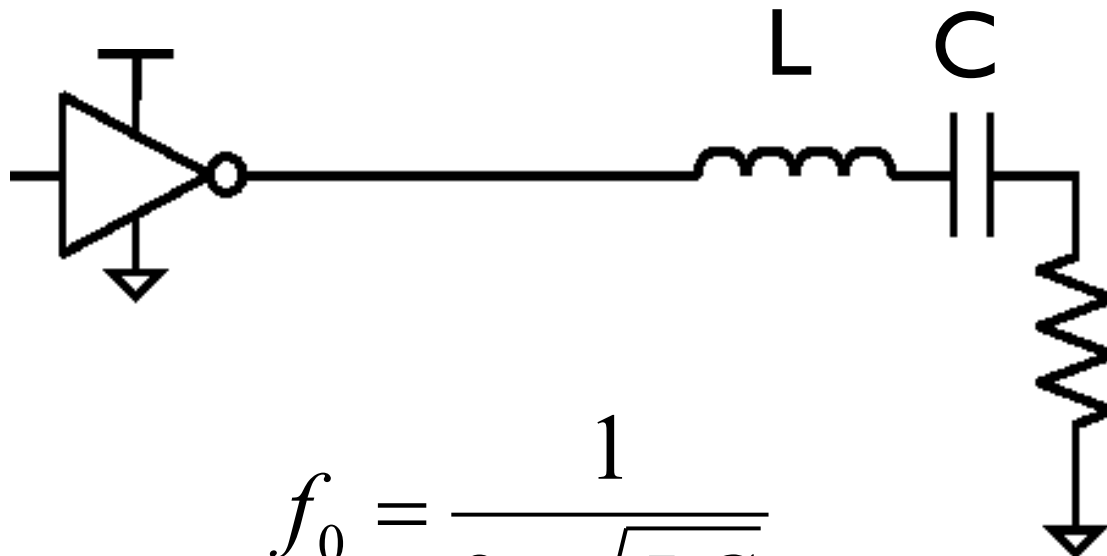


$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

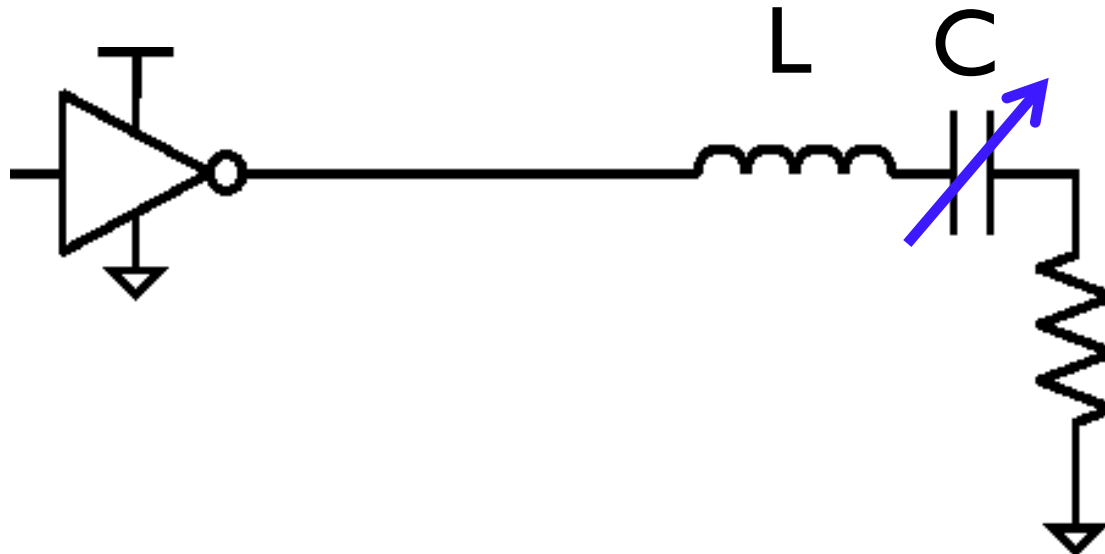
Would like to operate at (or near) resonance



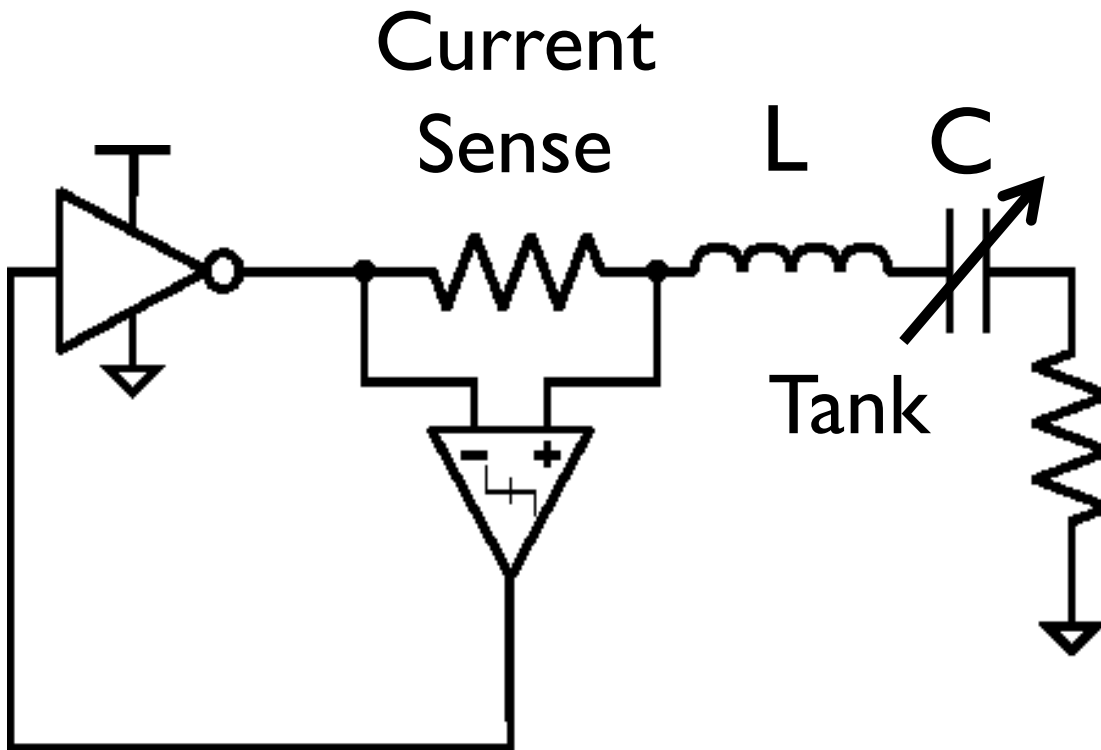But the capacitance depends on alignment and gap




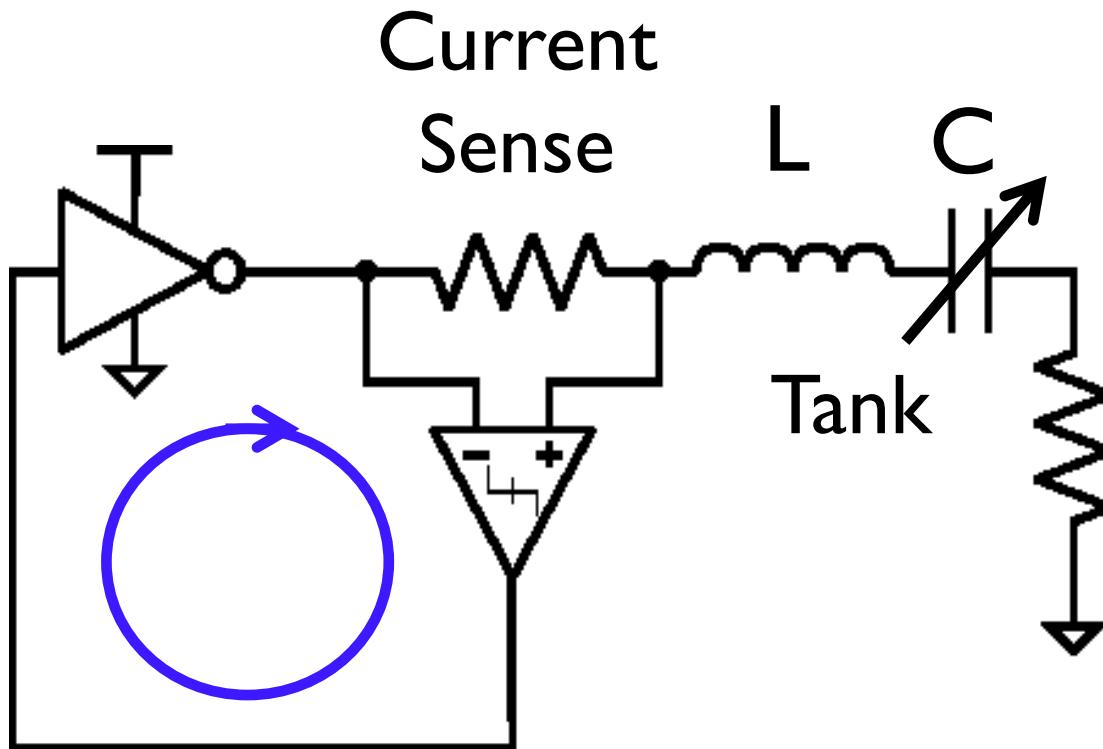Build an **oscillator** with L and C forming the tank




Phase shift around the loop = 0°

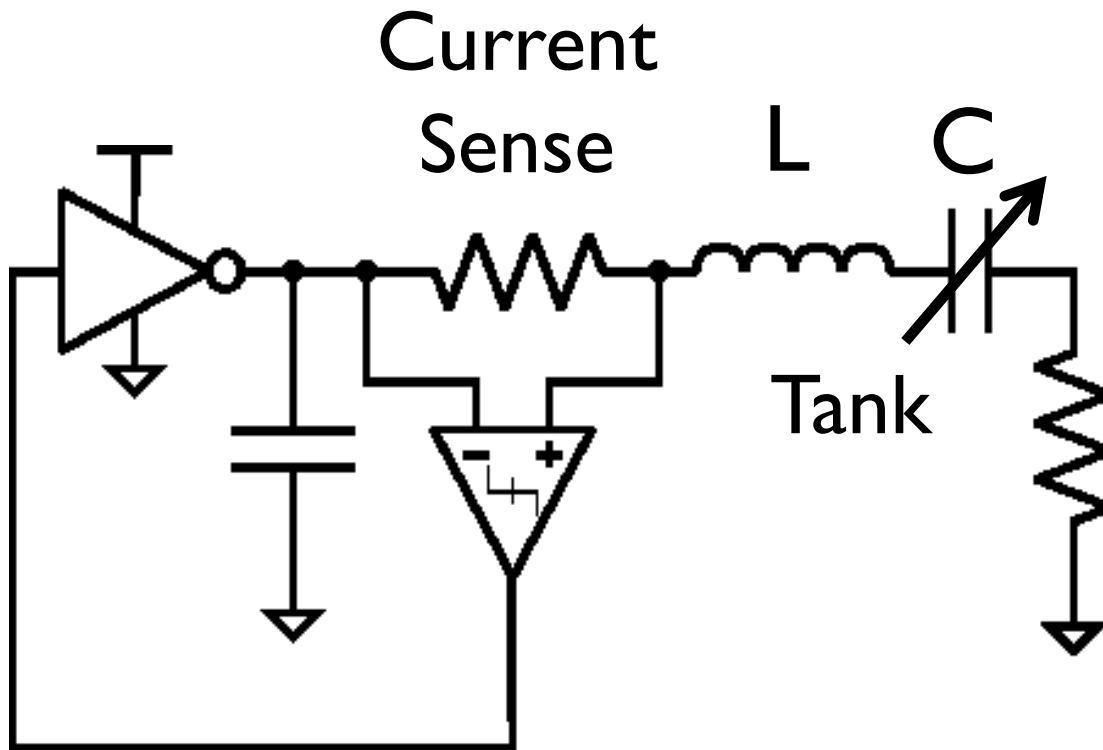
Current in tank forced in phase with drive voltage



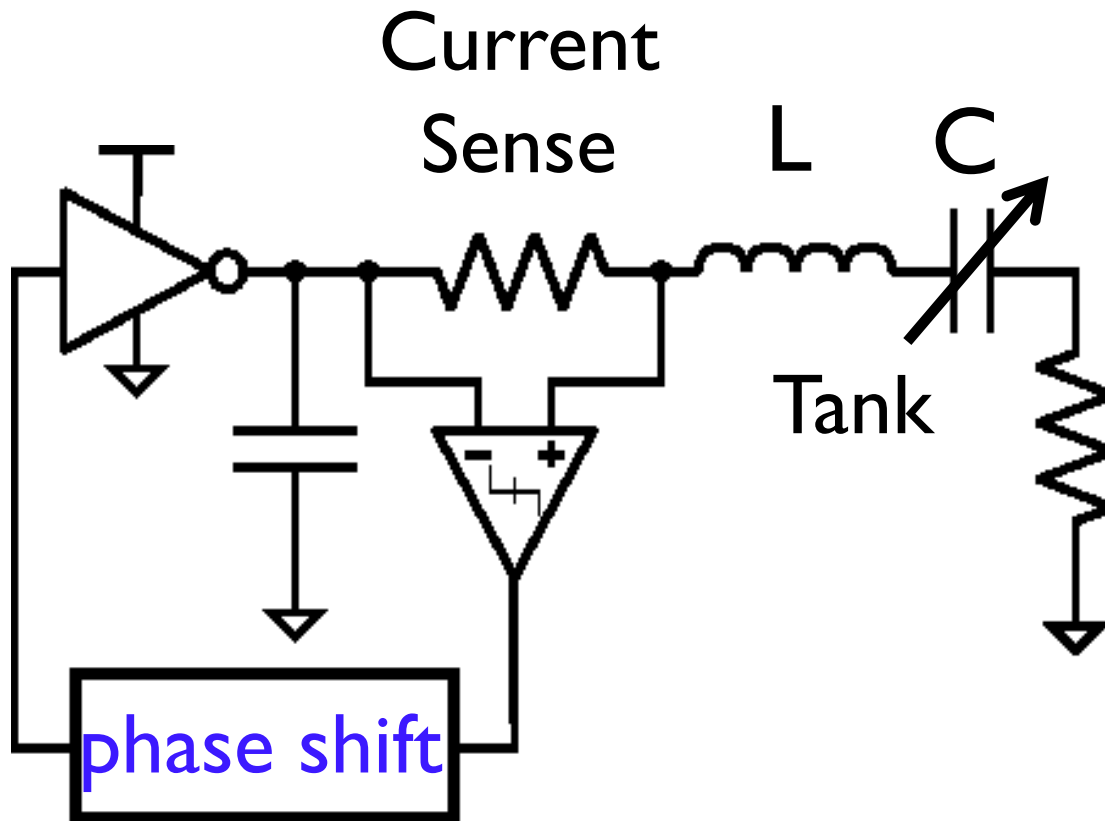
But we need to operate **above resonance**




Introduce **extra phase shift**

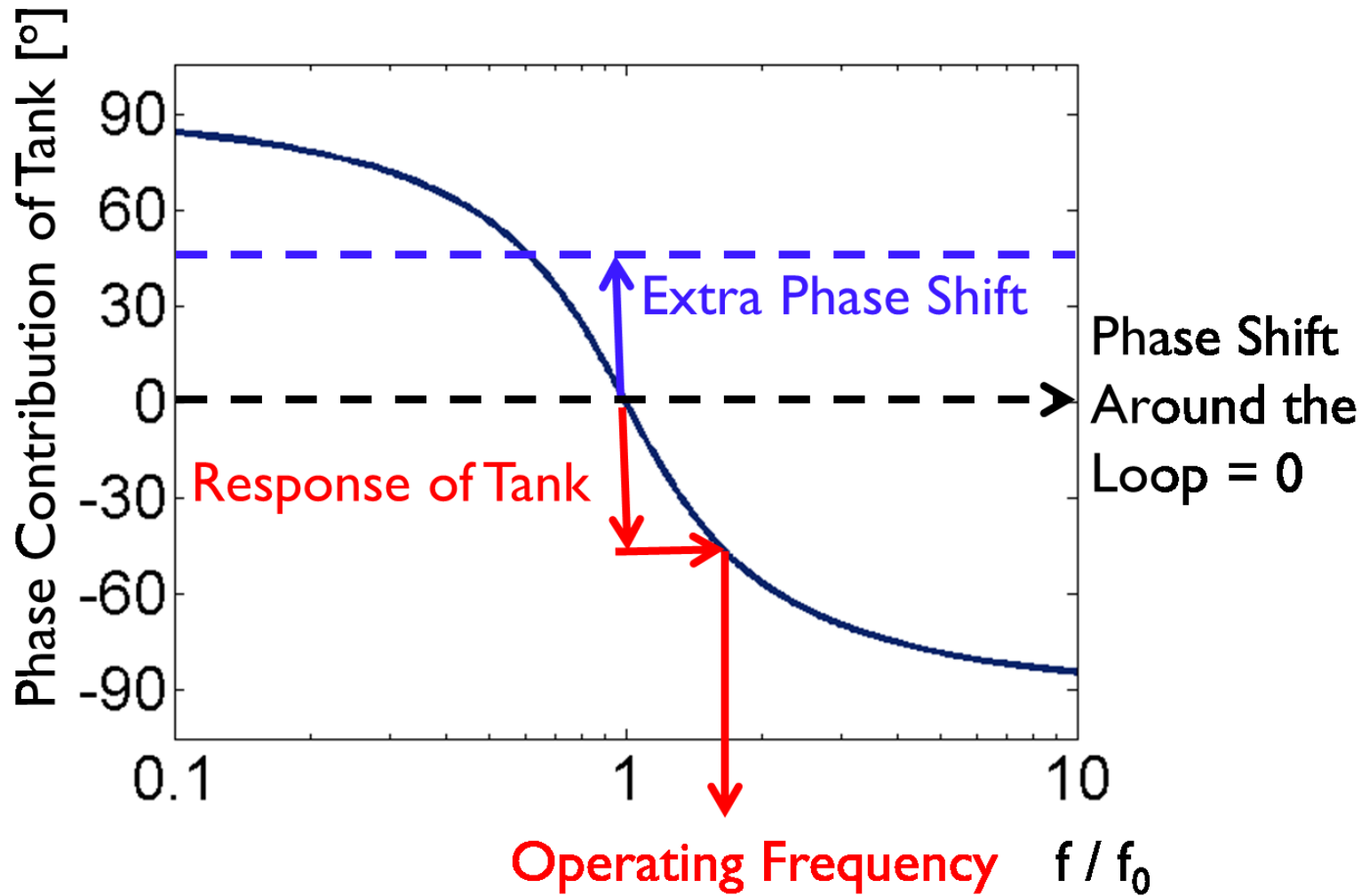


Adding phase shift changes the frequency

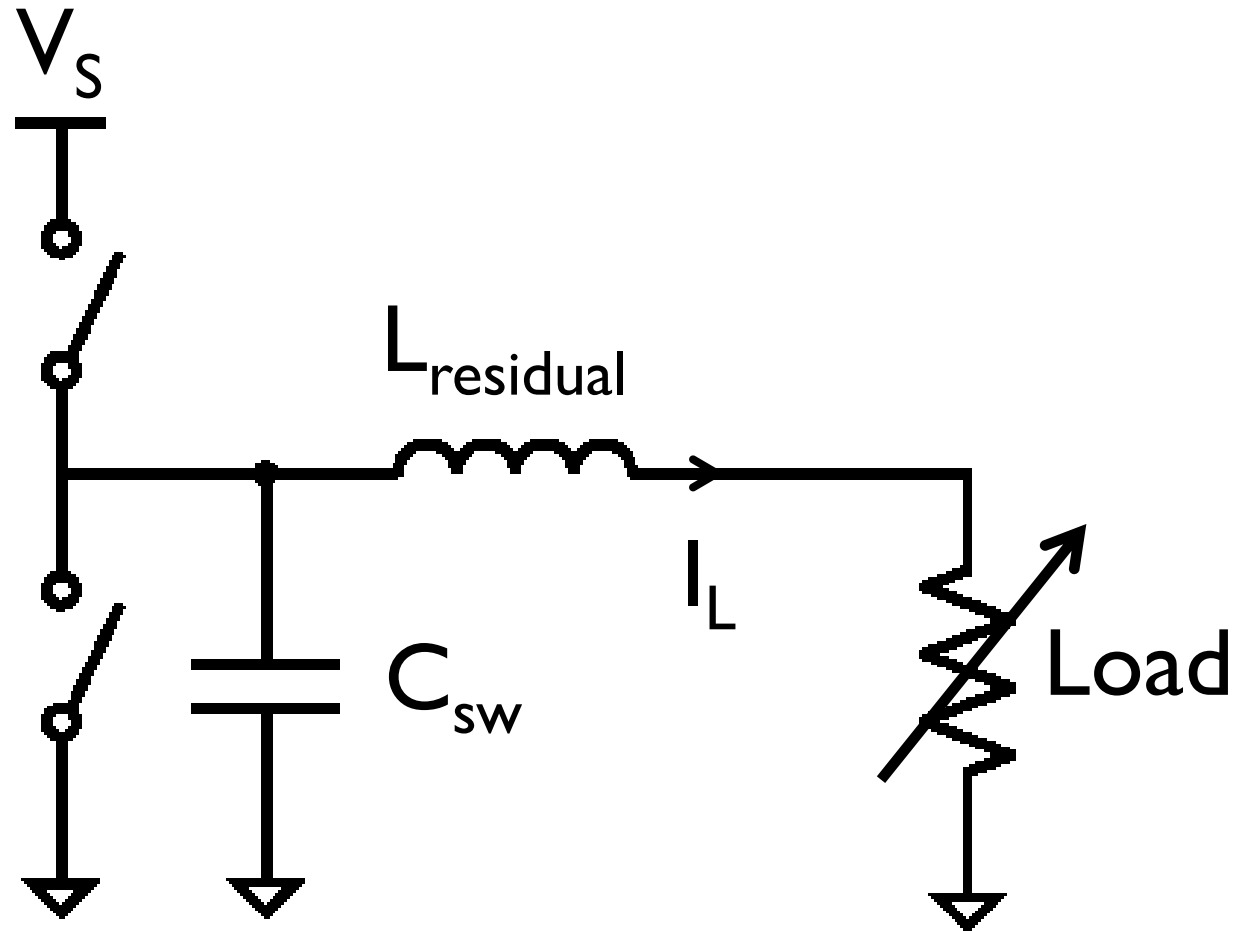

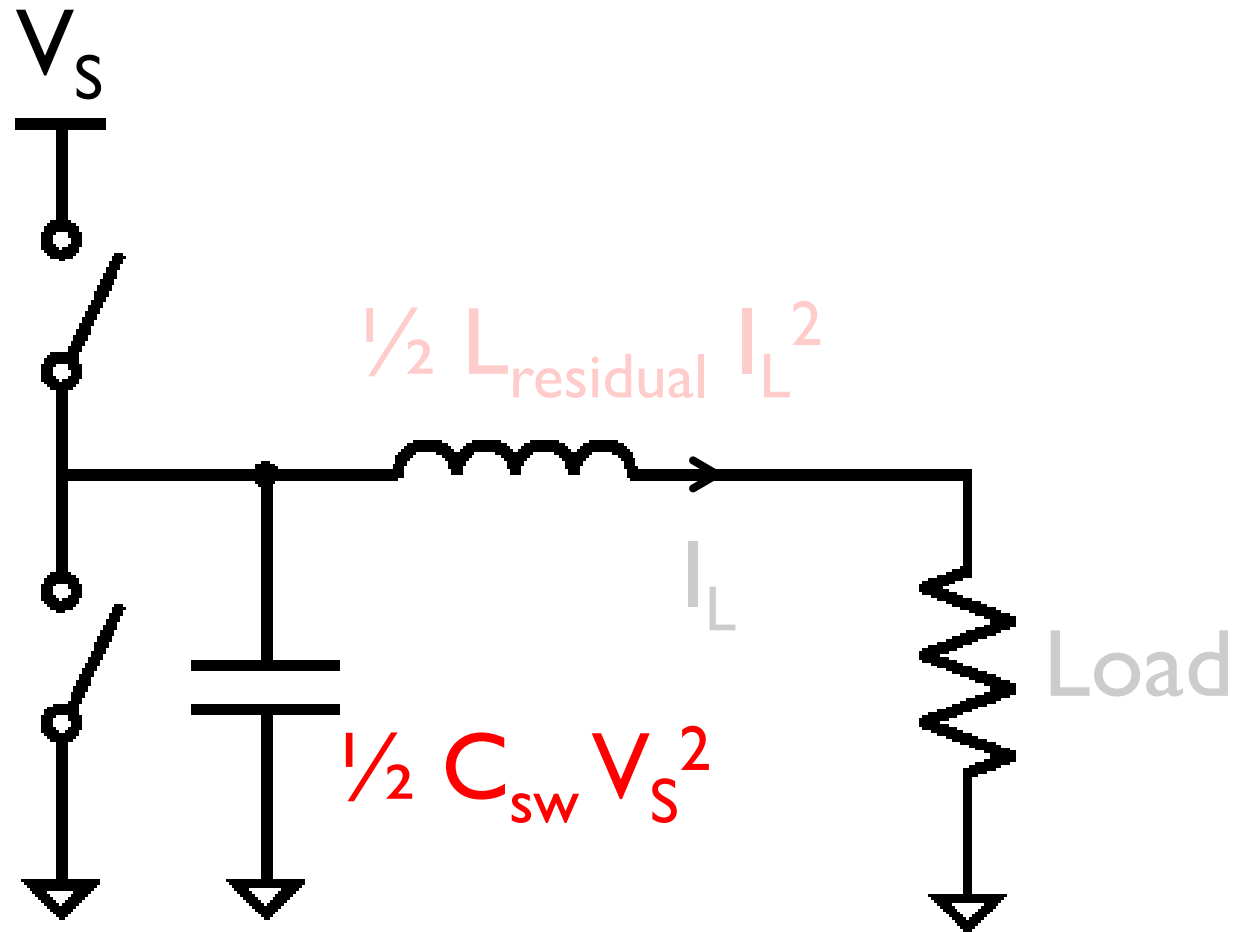The equivalent circuit above resonance (again)



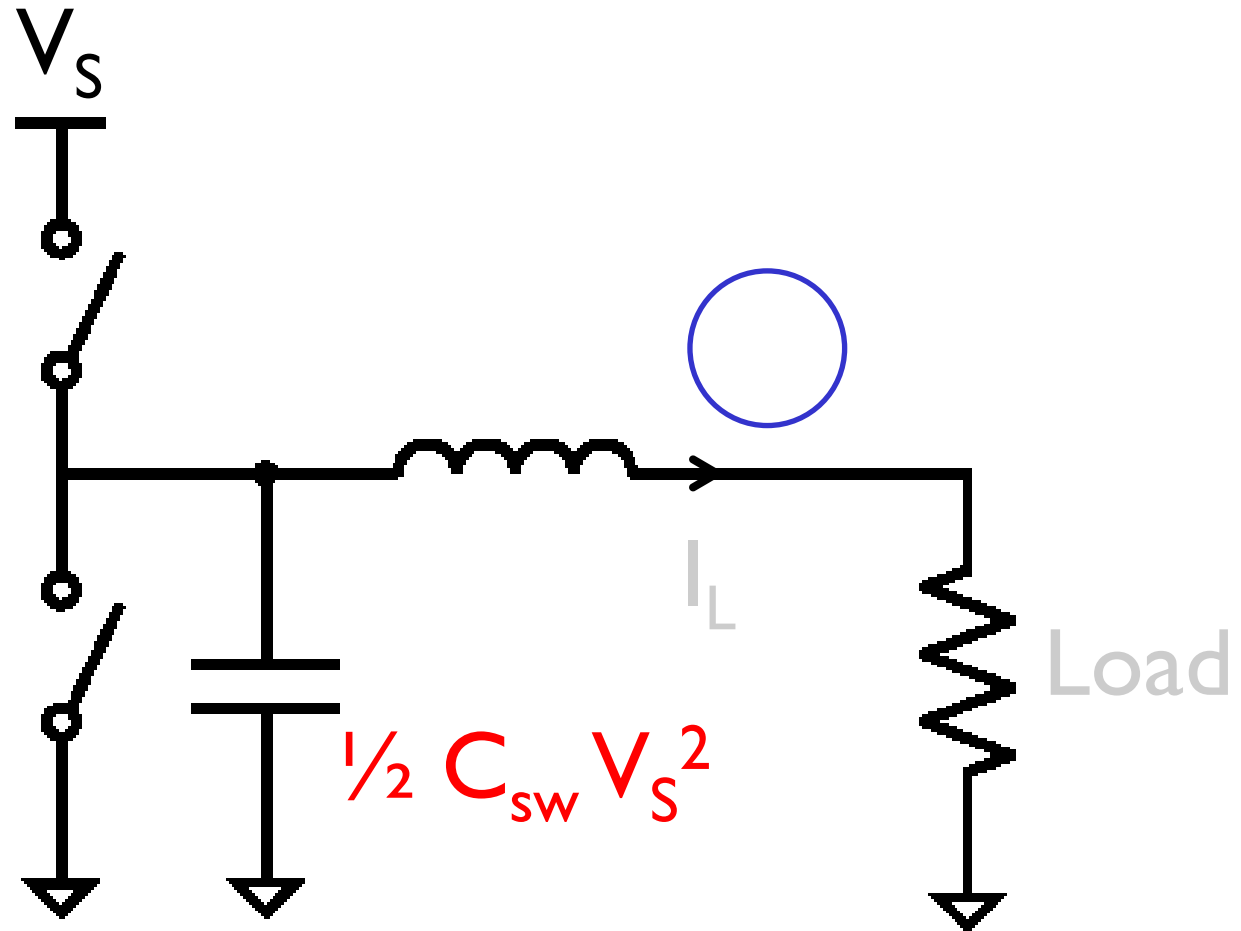
Light-load condition: not enough current in tank to get Zero Voltage Switching (ZVS)



Require a minimum I_L for ZVS

DC to AC

AC to DC

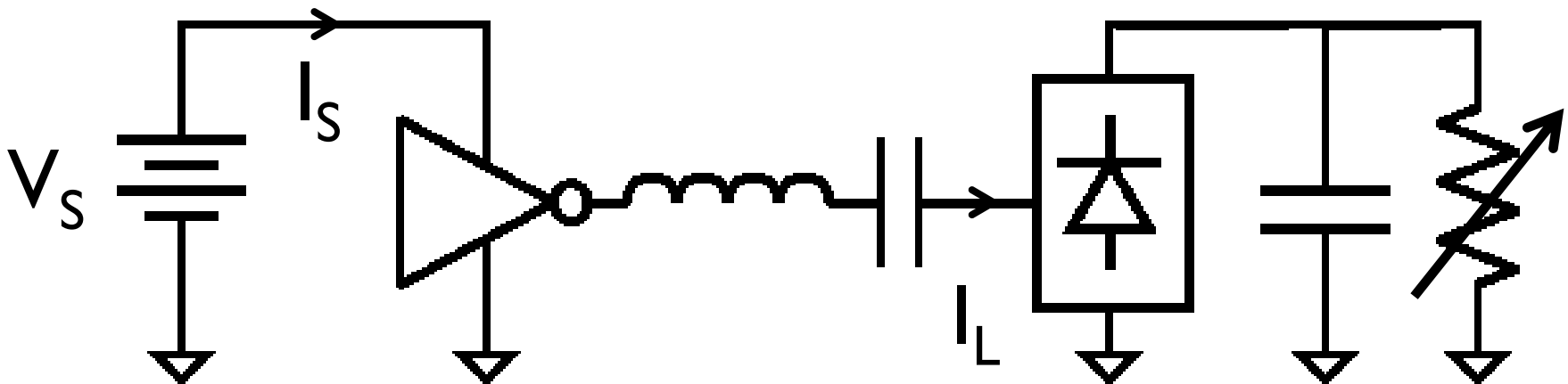


Filter
Capacitor

$I_S \approx I_L \Rightarrow$ Require a minimum I_S for ZVS

DC to AC


AC to DC

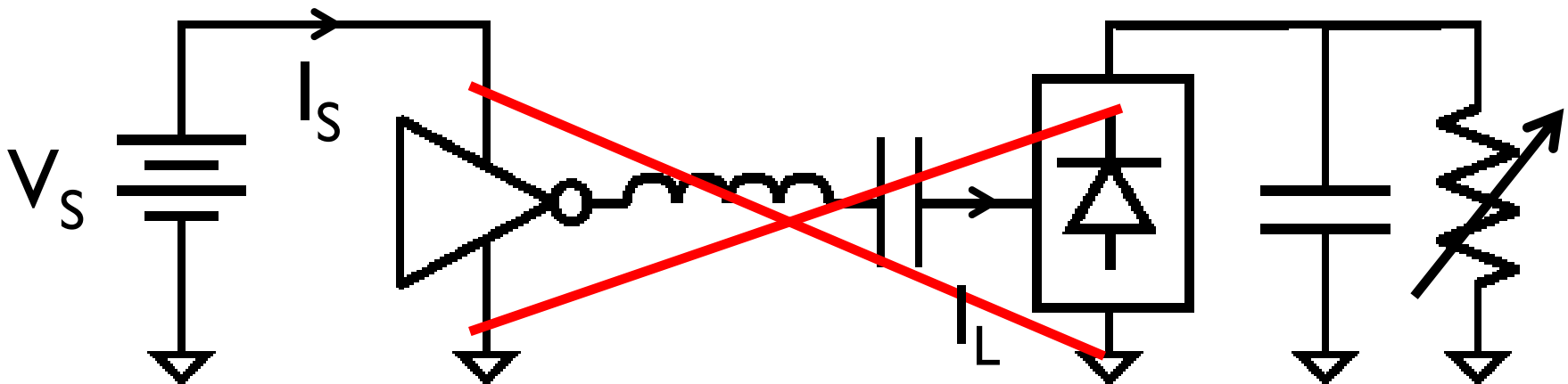

Filter
Capacitor


Can analyze this with a simple DC circuit

Variable Load

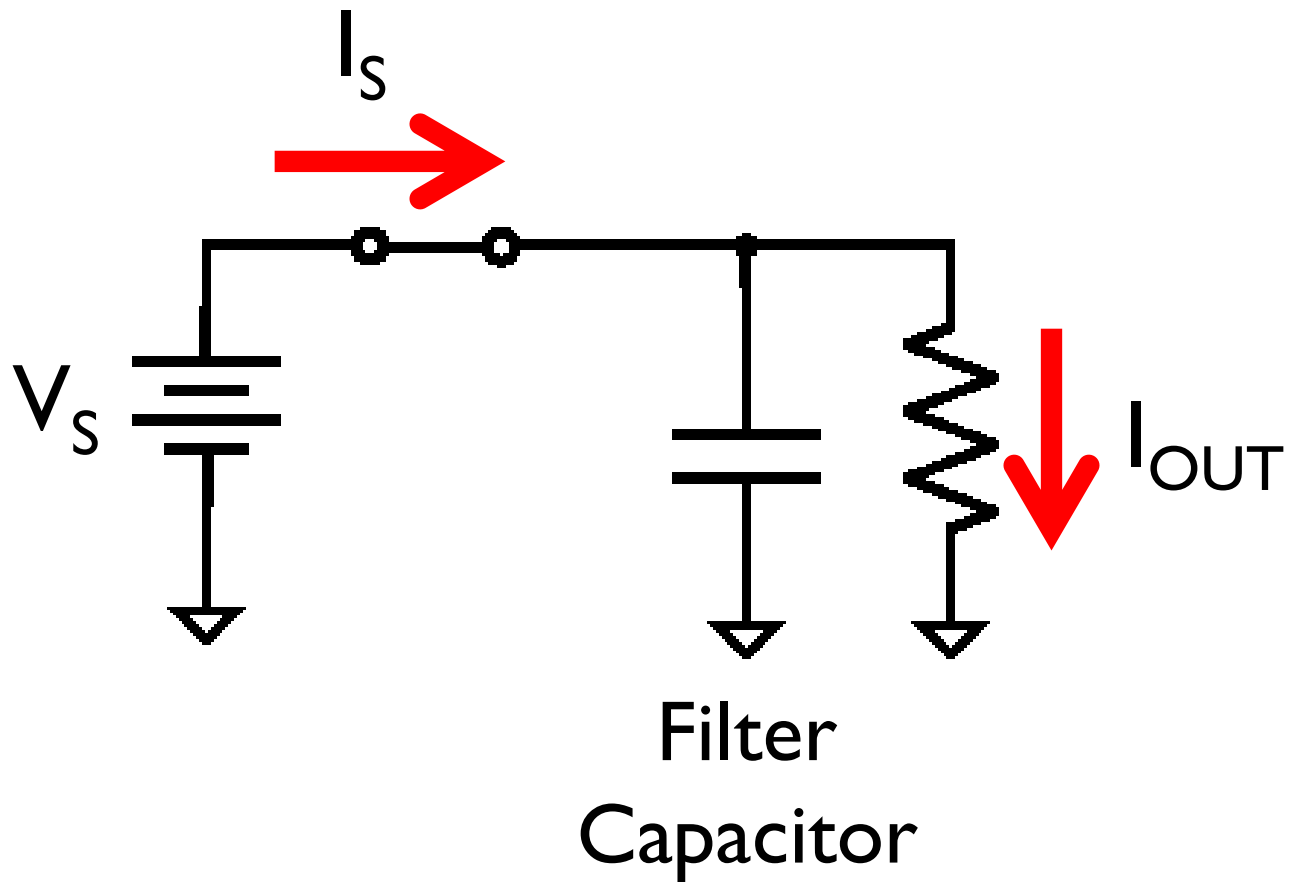


At full load, I_S is large

Variable Load

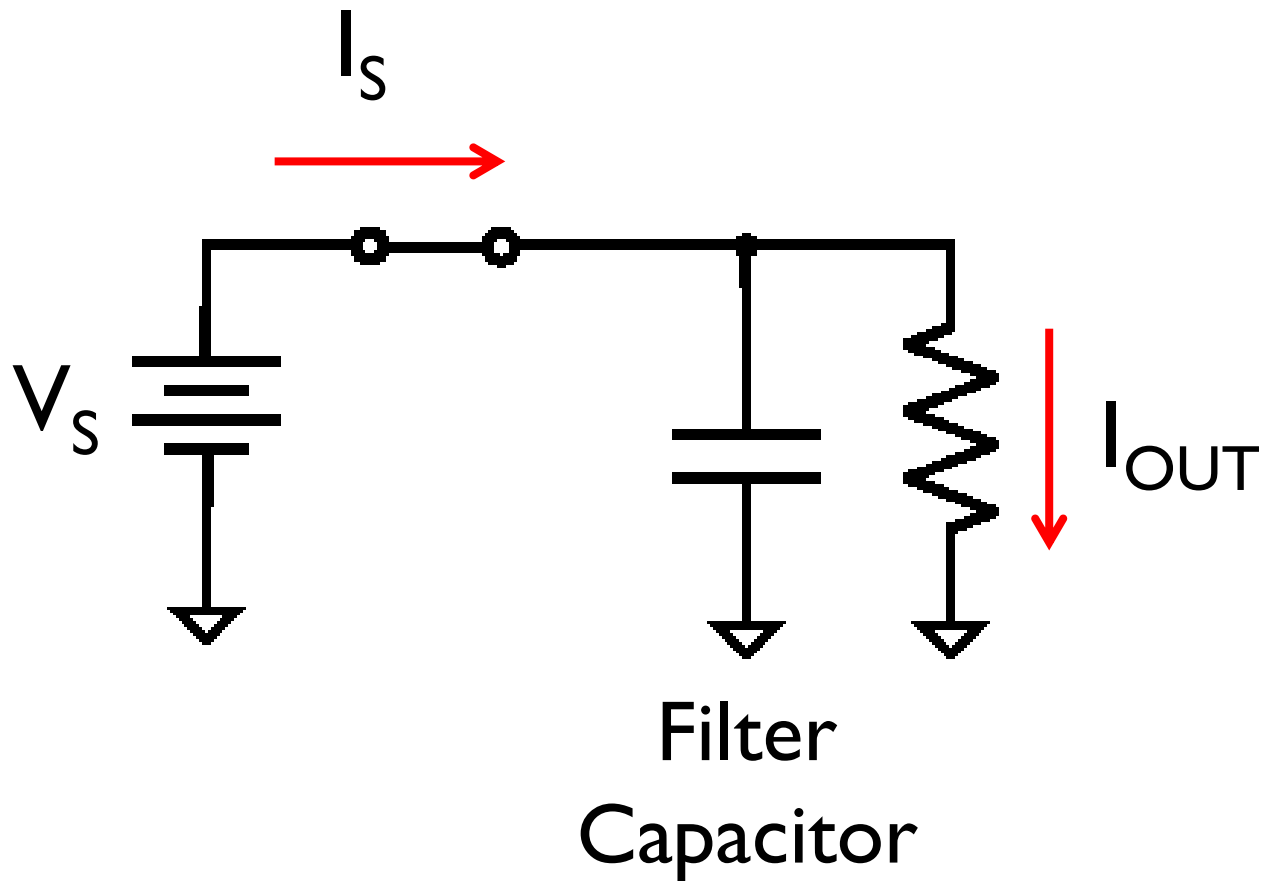

At light load, I_S is **too small**
Zero Voltage Switching is lost



Variable Load

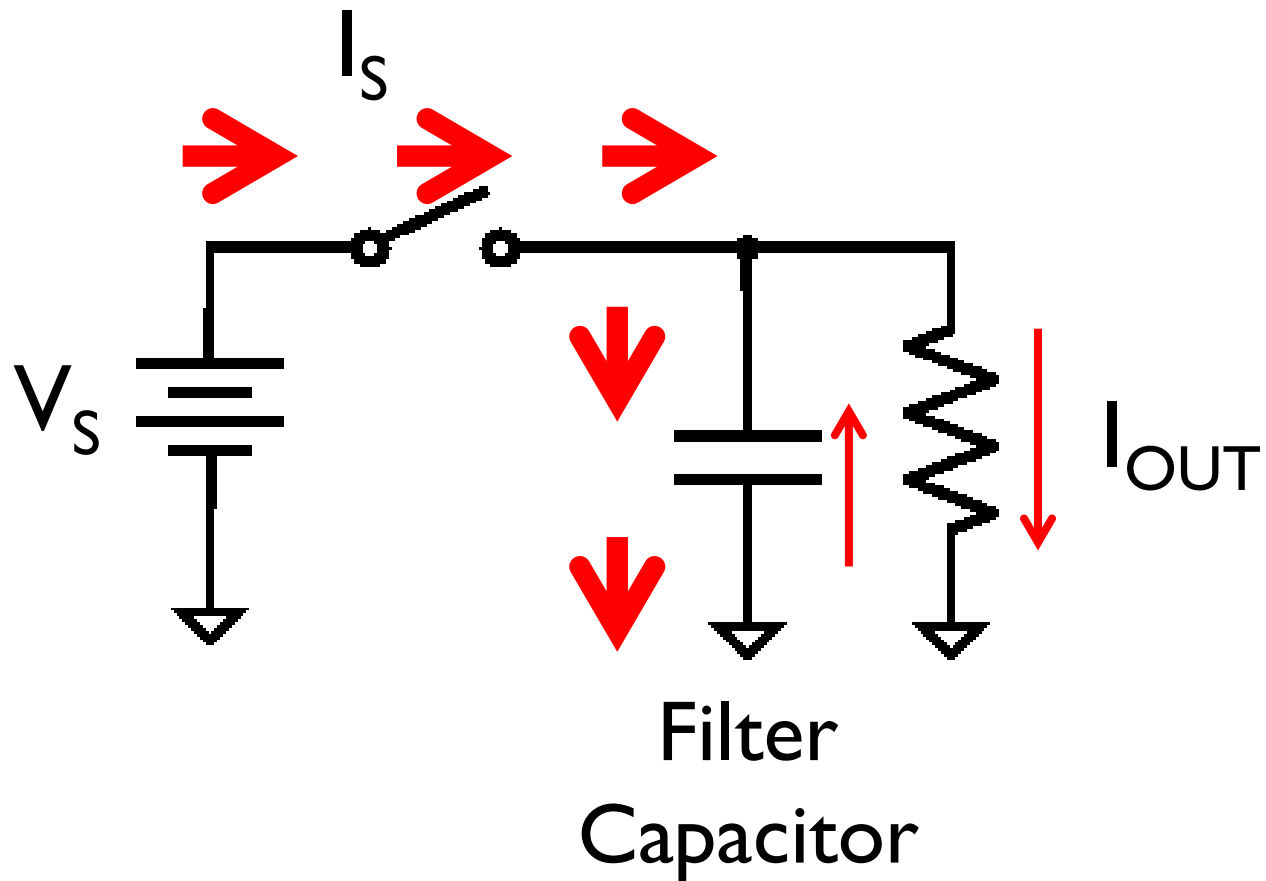


On/off modulation causes I_S to increase when driver is on: Zero Voltage Switching restored

What We Want

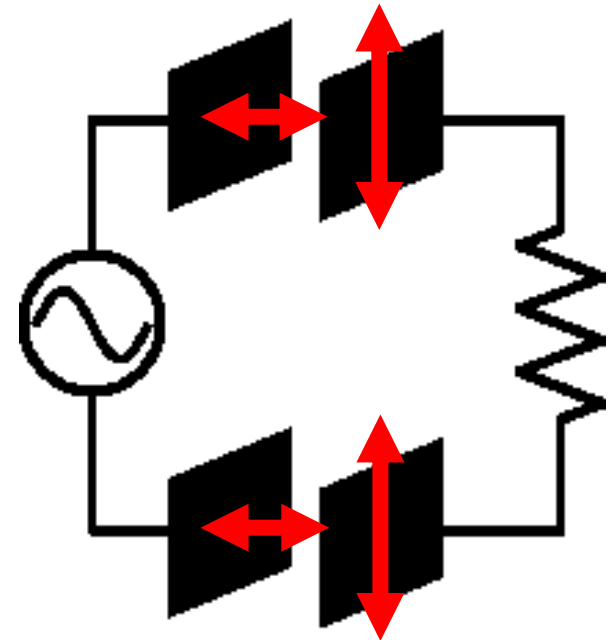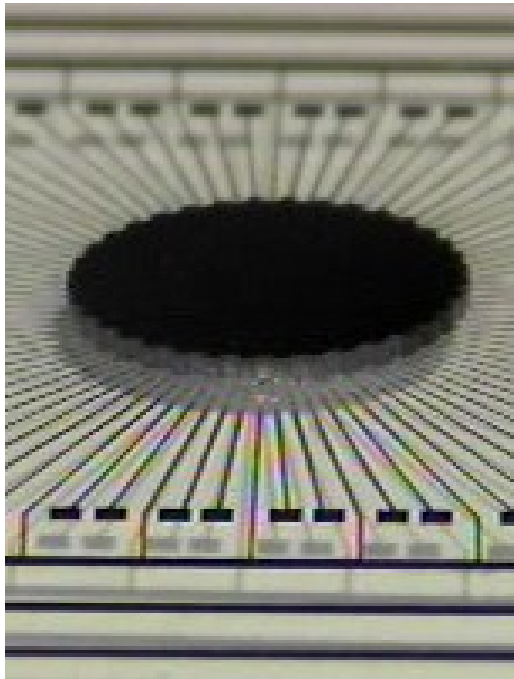
1 + 2 + 3
Small + **Efficient** + **Robust**



Capacitive Power Transfer System

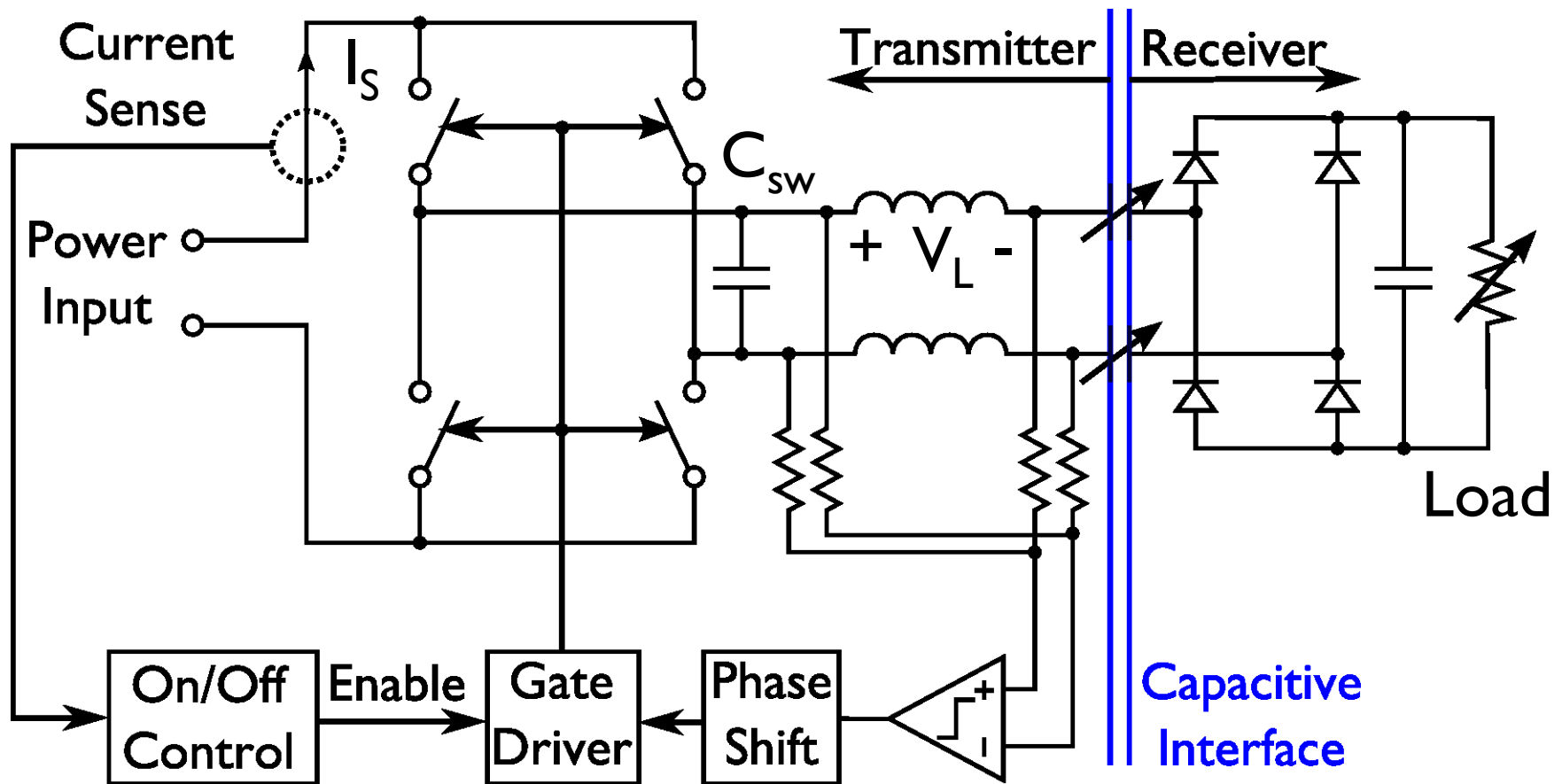

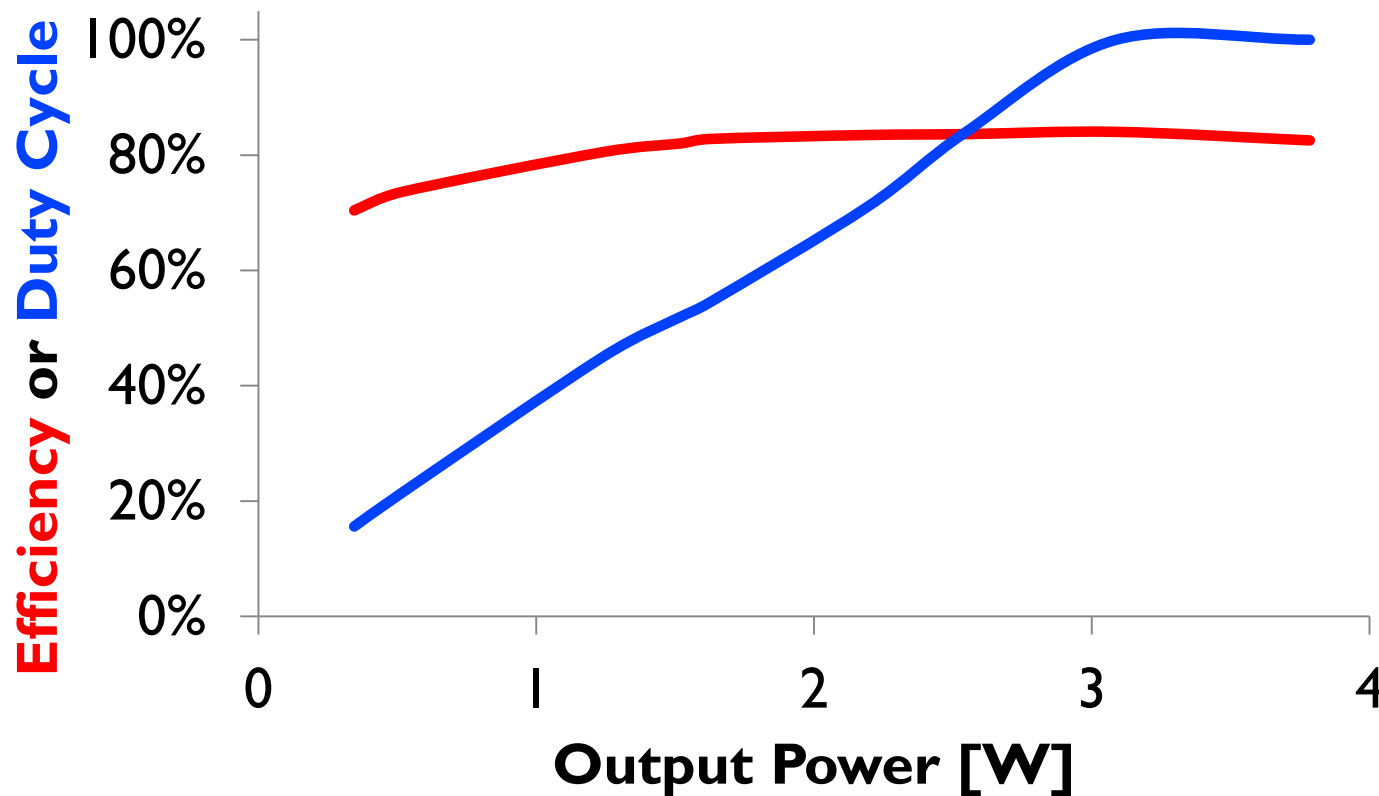With **6 by 10 cm²**, we transfer **3.8 W** at **83%** efficiency over a **0.5 mm** air gap.



How?

1. Resonant operation

Compensate for **small** coupling capacitance

2. Zero Voltage Switching

Improve the **efficiency**


3. Automatic Tuning

Robust to changes in coupling capacitance

4. Duty cycle adjustment without feedback from RX

Preserve efficiency at light loads

Capacitive Data Transfer

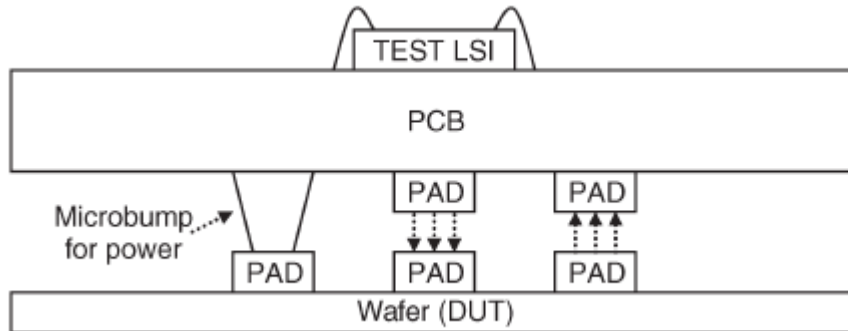

- 2 Gb/s data rate
- < 2 mW

Technology	0.18 μm CMOS	
Supply voltage	1.8 V	
Max. data rate	2 Gb/s	
Sensitivity	25 mV	
Input cap. (RX)	>600 fF	
BER	<10 ⁻¹⁰	
Core power @2 Gb/s	TX	4.87 μW
	RX	1.63 mW
Core area	TX	60 μm^2
	RX	2900 μm^2

G.-S. Kim, M. Takamiya, and T. Sakurai "A 25-mV-Sensitivity 2-Gb/s Optimum-Logic-Threshold Capacitive-Coupling Receiver for Wireless Wafer Probing Systems," TCAS II, Vol. 56, No. 9, Sept. 2009

Thank You!

Acknowledgements

Dr. Mei-Lin Chan

Dr. Simone Gambini

Prof. David Horsley

Dr. Mischa Megens

James Peng

Richard Przybyla

Kun Wang

Prof. Ming Wu

This material is based upon
work supported by the
Defense Advanced
Research Projects Agency
(DARPA) under Contract
No. W31P4Q-10-1-0002