Electronics for IoT

IoT Application

Bernhard E. Boser
University of California, Berkeley
boser@eecs.berkeley.edu

Outline

- Up to now:
 - Python
 - Circuits
 - Internet
- Today:
 - IoT Application

What should we build?

- Useful
- Representative
 - Combine key IoT concepts
 - "Model" for other IoT applications
 - The ones you invent
- Our first IoT app
 - Characterize solar cell

IoT App for Solar Cell Characterization

- Measure solar cell power as a function of load resistance
- Collect results
- Graph results and compute maximum power



Step 1: Measure I/V/P

- How can we measure solar cell voltage, current (and power) with the ESP32?
- We need a sensor!

Web Search

INA219 High Side DC Current Sensor Breakout - 26V ±3.2A Max ID ...

https://www.adafruit.com/product/904 *

Instead of struggling with two multimeters, you can just use the handy INA219B chip on this breakout to both measure both the high side voltage and DC current draw over I2C with 1% precision. ... Power the sensor itself with 3 to 5VDC and connect the two I2C pins up to your microcontroller.

INA220 26-V, Bi-Directional, Zero-Drift, Low- or High-Side, I2C Out ...

www.ti.com > ... > Current Sense Amplifiers > Current Sense Power / Current Monitors ▼
The INA220 is a current shunt and power monitor with an I²C- or SMBUS-compatible interface. The INA220 monitors both shunt drop and supply voltage. ... The separate shunt input on the INA220 allows it to be used in systems with low-side sensing. The INA220 is available in two grades: A and B.

LTC4151 - High Voltage I2C Current and Voltage Monitor - Linear ...

www.linear.com/product/LTC4151 *

Features. Wide Operating Voltage Range: 7V to 80V; 12-Bit Resolution for Both Current and Voltages; I²C Interface; Additional ADC Input Monitors an External Voltage; Continuous Scan and Snapshot Modes; Shutdown Mode (LTC4151) Reduces Quiescent Current to 120μA; Split SDA for Optolsolation ...

LTC2990 - Quad I2C Voltage, Current and Temperature Monitor ...

www.linear.com/product/LTC2990 *

Features. Measures Voltage, Current and Temperature; Measures Two Remote Diode Temperatures; ±0.5°C Accuracy, 0.06°C Resolution (Typ); ±1°C Internal Temperature Sensor (Typ); 14-Bit ADC Measures Voltage/Current; 3V to 5.5V Supply Operating Voltage; Four Selectable Addresses; Internal 10ppm/°C Voltage ...

SparkFun Current Sensor Breakout - INA169 - SEN-12040 - SparkFun ...

https://www.sparkfun.com/products/12040 *

The INA169 is definitely a cheaper chip, and using a microcontroller's ADC isn't all that bad (you also get to use 1 pin instead of 2). From an Arduino perspective, that's an analogRead() vs. the initialization of the Wire/I2C library. That being said, if there is enough interest for an I2C current sensor, please let us know! It would ...

Power/Current Sensors - Microchip

www.microchip.com/powercurrentsensors *

EMC1701-1, Samples Available, \$0.76, Current/DC Power Sensor with Temperature Monitoring, 10, 20, 40, 80, \pm 1, 2.5 to 2600, +3 to +24, 1, 0, \pm 0.25 / \pm 1.0, 2, Hardware, SMBus/I2C, yes, 12/QFN. EMC1701-2, In Production, \$0.65, Current/DC Power Sensor with Temperature Monitoring, 10, 20, 40, 80, \pm 1, 2.5 to 2600, +3 to ...


- Lot's of options
- Any suitable for our needs?
- How are we going to find out



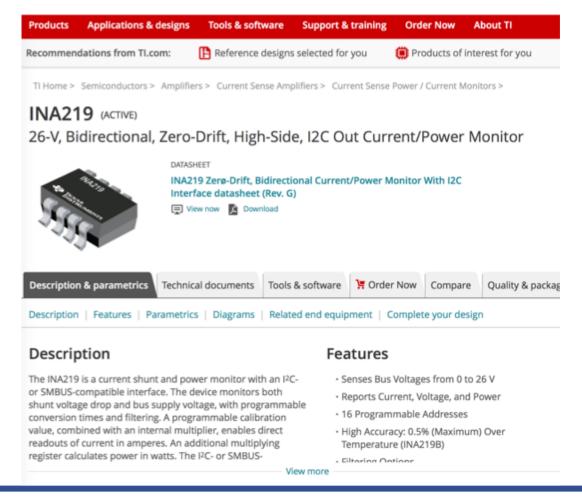B. E. Boser IoT49: IoT Application

INA 219 Manufacturer Website

Download datasheet from manufacturer website (TI)





INA219 Datasheet



INA219

SBOS448G - AUGUST 2008-REVISED DECEMBER 2015

INA219 Zerø-Drift, Bidirectional Current/Power Monitor With I²C Interface

1 Features

- Senses Bus Voltages from 0 to 26 V
- · Reports Current, Voltage, and Power
- 16 Programmable Addresses
- High Accuracy: 0.5% (Maximum) Over Temperature (INA219B)
- Filtering Options
- Calibration Registers
- SOT23-8 and SOIC-8 Packages

2 Applications

- Servers
- Telecom Equipment
- Notebook Computers
- Power Management
- Battery Chargers
- Welding Equipment
- Power Supplies
- Test Equipment

3 Description

The INA219 is a current shunt and power monitor with an I^2C - or SMBUS-compatible interface. The device monitors both shunt voltage drop and bus supply voltage, with programmable conversion times and filtering. A programmable calibration value, combined with an internal multiplier, enables direct readouts of current in amperes. An additional multiplying register calculates power in watts. The I^2C - or SMBUS-compatible interface features 16 programmable addresses.

The INA219 is available in two grades: A and B. The B grade version has higher accuracy and higher precision specifications.


The INA219 senses across shunts on buses that can vary from 0 to 26 V. The device uses a single 3- to 5.5-V supply, drawing a maximum of 1 mA of supply current. The INA219 operates from -40°C to 125°C.

Device Information(1)

PART NUMBER	PACKAGE	BODY SIZE (NOM)
INIA 240	SOIC (8)	3.91 mm × 4.90 mm
INA219	SOT-23 (8)	1.63 mm × 2.90 mm

 For all available packages, see the orderable addendum at the end of the data sheet.

INA219 "Simplified Schematic"

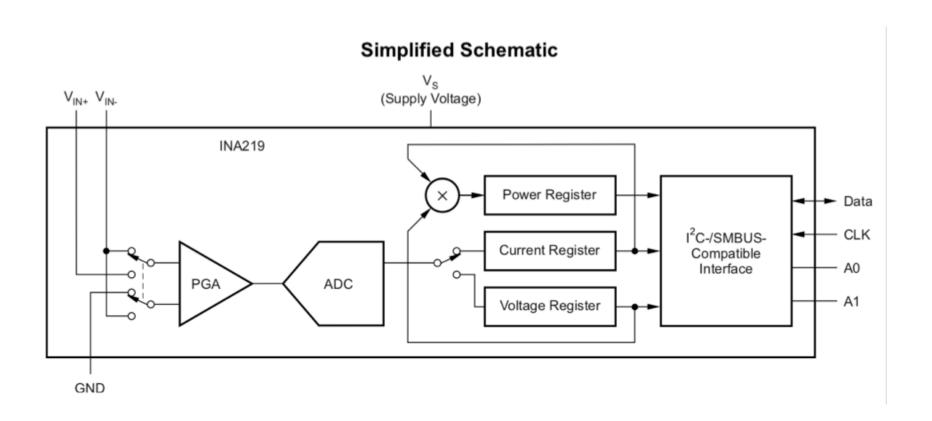



INA219 Configured

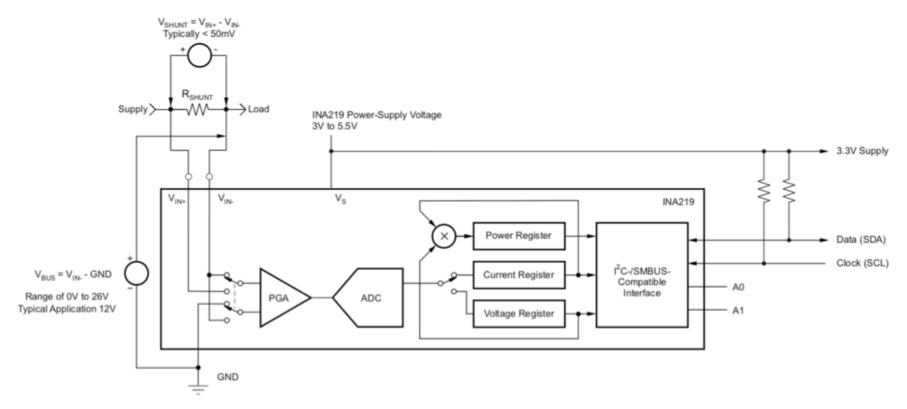


Figure 13. INA219 Configured for Shunt and Bus Voltage Measurement

Let's Redraw this a little ...


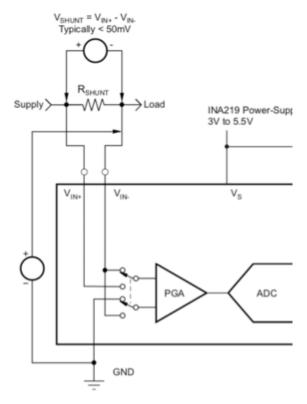


Figure 13. INA219 Configure

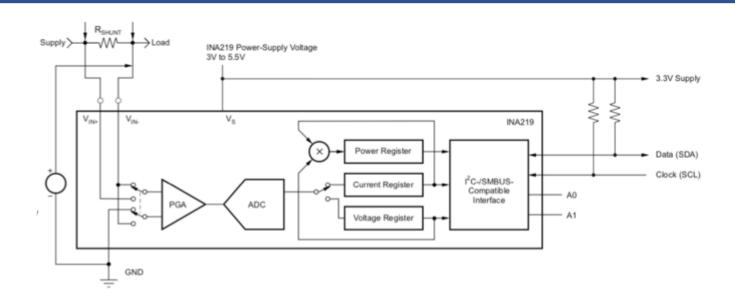

Hooking this up to the ESP32



Just 4 wires:

- Data (SDA)
- Clock (SCL)
- 3.3V supply (Huzzah32 generates this)
- GND



Huzzah32

GPIO ALT μ**Py**

RESET
3.3V


	GND		4
26	DAC2	Α0	5
25	DAC1	A1	6
34	ADC6	A2	7
39	ADC3	A3	8
36	ADC0	A4	9
4		A5	10
5	SCK	A16	11
18	MOSI	A17	12
19	MISO	A18	13
16		A19	14
		A20	15
17		AZU	
17 21		A21	16




μ**Py** ALT GPIO

28		VBAT					
27	EN 3.3V						
26	VUSB						
25	A12	LED	13				
24	A11	BOOT	12				
23	A10		27				
22	A9	ADC5	33				
21	A8		15				
20	Α7	ADC4	32				
19	A6		14				
18	A15	SCL	22				
17	A14	SDA	23				


Real INA219

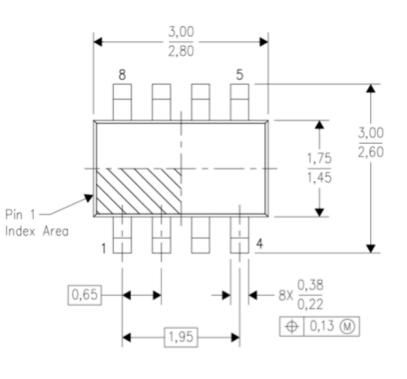


- This thing is tiny
- "big" pepper corn

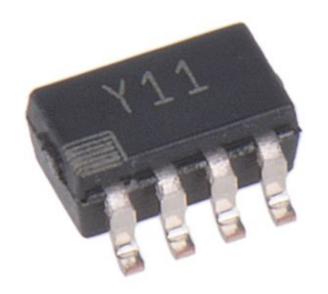

Hone your soldering skills ...

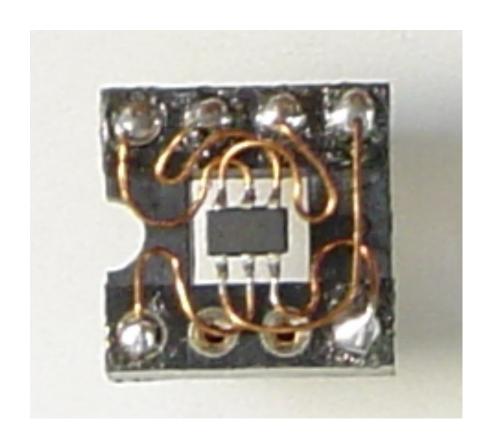

Or get a breakout board ...

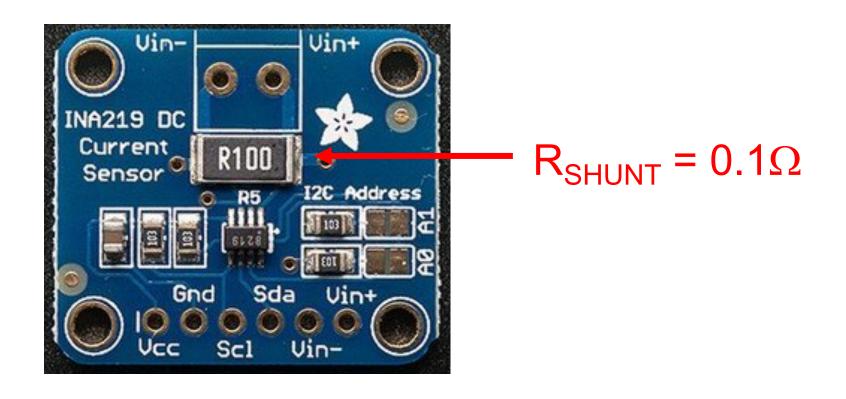

- https://www.adafruit.com/product/904
- In your "goodies" bag ...



More datasheet ...

7.1 Absolute Maximum Ratings

over operating free-air temperature range (unless otherwise noted)(1)

		MIN	MAX	UNIT
Vs	Supply voltage		6	V
Analog Inputs	Differential (V _{IN+} – V _{IN-}) ⁽²⁾	-26	26	V
IN+, IN-	Common-mode(V _{IN+} + V _{IN-}) / 2	-0.3	26	V
SDA		GND - 0.3	6	V
SCL		GND - 0.3	V _S + 0.3	V
Input current int	o any pin		5	mA
Open-drain digital output current			10	mA
Operating temp	erature	-40	125	°C
T _J	Junction temperature		150	°C
T _{stg}	Storage temperature	-65	150	°C

⁽¹⁾ Stresses beyond those listed under Absolute Maximum Ratings may cause permanent damage to the device. These are stress ratings only, which do not imply functional operation of the device at these or any other conditions beyond those indicated under Recommended Operating Conditions. Exposure to absolute-maximum-rated conditions for extended periods may affect device reliability.

⁽²⁾ V_{IN+} and V_{IN-} may have a differential voltage of -26 to 26 V; however, the voltage at these pins must not exceed the range -0.3 to 26 V.

Electrical Characteristics

7.5 Electrical Characteristics:


At T_A = 25°C, V_e = 3.3 V, V_{NA} = 12V, V_{NA} = (V_{NA} - V_{NA}) = 32 mV, PGA = /1, and BRNG⁽¹⁾ = 1, unless otherwise noted.

		TEST CONDITIONS	INA219A) = 1, unless otherwise not INA219B			
	PARAMETER		MIN	TYP	MAX	MIN	TYP	MAX	UNIT
INPUT									
		PGA = /1	0		±40	0		±40	mV
	Full-scale current sense (input) voltage	PGA = /2	0		±80	0		±80	mV
V _{SHUNT}	range	PGA = /4	0		±160	0		±160	mV
		PGA = /8	0		±320	0		±320	mV
	2	BRNG = 1	0		32	0		32	V
	Bus voltage (input voltage) range ⁽²⁾	BRNG = 0	0		16	0		16	V
CMRR	Common-mode rejection	V _{IN+} = 0 to 26 V	100	120		100	120		dB
		PGA = /1		±10	±100		±10	±50 ⁽⁴⁾	μV
		PGA = /2		±20	±125		±20	±75 ⁽⁴⁾	μV
Vos	Offset voltage, RTI ⁽³⁾	PGA = /4		±30	±150		±30	±75 ⁽⁴⁾	μV
		PGA = /8		±40	±200		±40	±100 ⁽⁴⁾	μV
	vs Temperature	T _A = -25°C to 85°C		0.1			0.1		μV/°C
PSRR	vs Power Supply	V _S = 3 to 5.5 V		10			10		μV/V
	Current sense gain error			±40			±40		m%
	vs Temperature	T _A = -25°C to 85°C		1			1		m%/"
	IN+ pin input bias current	Active mode		20			20		μА
	IN- pin input bias current V _{IN-} pin input impedance	Active mode		20 320			20 320		μA kΩ
	IN+ pin input leakage (5)	Power-down mode		0.1	±0.5		0.1	±0.5	μА
	IN- pin input leakage (5)	Power-down mode		0.1	±0.5		0.1	±0.5	μA
DC ACC	URACY								
	ADC basic resolution			12			12		bits
	Shunt voltage, 1 LSB step size			10			10		μV
	Bus voltage, 1 LSB step size			4			4		mV
	Current measurement error			±0.2%	±0.5%		±0.2%	±0.3%(
	over Temperature	T _A = -25°C to 85°C			±1%			±0.5%(
	Bus voltage measurement error			±0.2%	±0.5%		±0.2%	±0.5%	
	over Temperature	T _A = -25°C to 85°C			±1%			±1%	
	Differential nonlinearity			±0.1			±0.1		LSB
ADC TIN	MING								
		12 bit		532	586		532	586	μs
		11 bit		276	304		276	304	μs
	ADC conversion time	10 bit		148	163		148	163	μs
		9 bit		84	93		84	93	μs
	Minimum convert input low time		4			4			μs

 Needed to write software driver

B. E. Boser IoT49: IoT Application 18

Someone has already done the work!

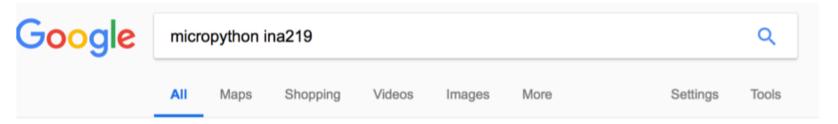

About 12,100 results (0.54 seconds)

Micropython library for the TI INA219 voltage/current sensor ...

https://forum.micropython.org > ... > Drivers for External Components ▼

May 16, 2017 - https://github.com/chrisb2/pyb_ina219. I have written this library based on one I wrote for the Raspberry Pi. It supports the INA219 voltage, current and power monitor sensor from Texas Instruments. The intent of the library is to make it easy to use the quite complex functionality of this sensor. Its currently ...

MicroPython on ESP32 with SPIRAM support - Page 25Jan 10, 2018Lolin32 Battery StateAug 14, 2017boot.py not executedAug 2, 2017Micropython driver for TI INA219?Dec 7, 2016

More results from forum.micropython.org


GitHub - chrisb2/pyb_ina219: This library for the MicroPython makes it ... https://github.com/chrisb2/pyb_ina219 ▼

pyb_ina219 - This library for the **MicroPython** makes it easy to leverage the complex functionality of the Texas Instruments **INA219** sensor to measure voltage, current and power.

You've visited this page 4 times. Last visit: 1/12/18



INA219 on Github

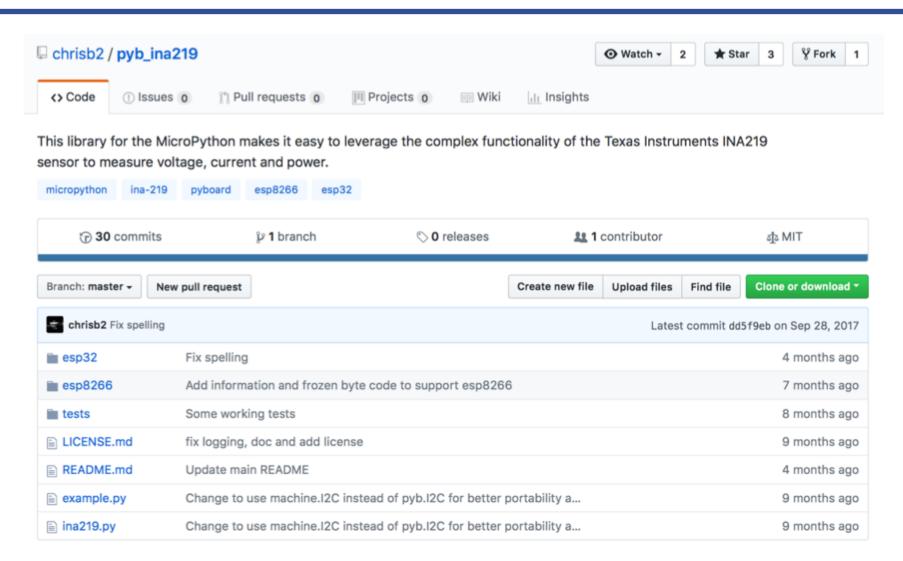



INA219 Driver Usage Instructions

Usage

If you want to give it a try then copy *ina219.py* onto the flash drive of your pyboard, connect the sensor to the I2C(1) or I2C(2) interfaces on the pyboard, then from a REPL prompt execute:

```
from ina219 import INA219
from machine import I2C

I2C_INTERFACE_N0 = 2
SHUNT_OHMS = 0.1

ina = INA219(SHUNT_OHMS, I2C(I2C_INTERFACE_N0))
ina.configure()
print("Bus Voltage: %.3f V" % ina.voltage())
print("Current: %.3f mA" % ina.current())
print("Power: %.3f mW" % ina.power())

Depends on MicroPython port
See next page
```

https://github.com/chrisb2/pyb_ina219

INA219 Example

```
from ina219 import INA219
from machine import I2C, Pin
from board import SDA, SCL
import time
i2c = I2C(id=0, scl=Pin(SCL), sda=Pin(SDA), freq=100000)
# optional: detect all devices connected to I2C bus
print("scanning I2C bus ...")
print("I2C:", i2c.scan())
# initialize INA219
SHUNT_RESISTOR_OHMS = 0.1
ina = INA219(SHUNT_RESISTOR_OHMS, i2c)
ina.configure()
# read measurements
while True:
    v = ina.voltage()
    i = ina.current()
    p = ina.power()
    print("V = {:6.2f}, I = {:6.2f}, P = {:6.2f}".format(v, i, p))
    time.sleep(0.5)
```

Circuit


- Solar cell characterization
- Components:
 - 1.
 - 2.
 - 3.
 - 4.


Approach

- Symbols
- Circuit diagram
- Optional: wiring diagram




INA219 Symbol

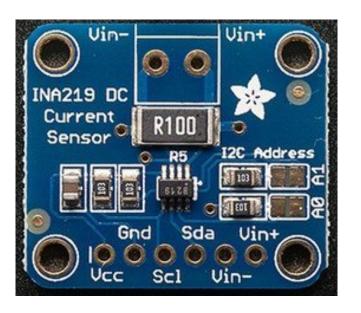

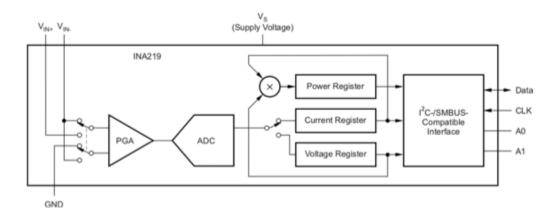

25

ESP32

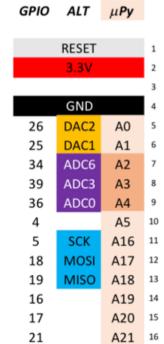




μ**Py** ALT GPIO

28	VBAT						
27	EN 3.3V						
26		VUSB					
25	A12	LED	13				
24	A11	BOOT	12				
23	A10		27				
22	A9	ADC5	33				
21	A8		15				
20	Α7	ADC4	32				
19	A6		14				
18	A15	SCL	22				
17	A14	SDA	23				

Circuit Diagram




Wiring Diagram

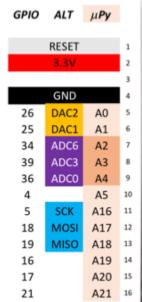




場でま 1111 1113 111				
2 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1 1	28		VBAT	
P huzzah!	27		EN 3.3V	
28	26		VUSB	
Seceseses	25	A12	LED	13
1 12	24	A11	BOOT	12
	23	A10		27
	22	A9	ADC5	33
	21	A8		15
	20	Α7	ADC4	32
70 (1990 hassa (EU)) (9	19	A6		14
	18	A15	SCL	22
9	17	A14	SDA	23
SOA				

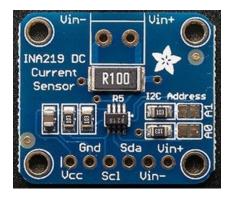





Complete Circuit

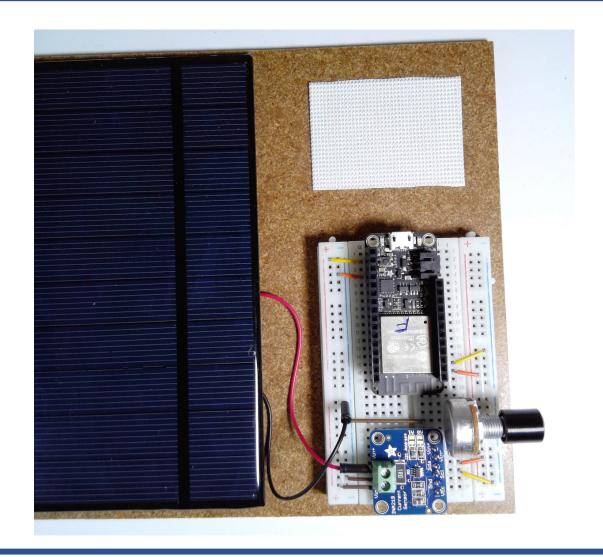

Testing

```
2606.30hm
V =
     5.13V,
                    1.97mA,
                                     10mW,
               P =
V =
     5.16V,
                    2.10mA,
                                     11mW,
                                                 2461,90hm
                V =
     5.18V,
                                                 1989.50hm
                    2.60mA,
                                     13mW,
V =
     5.14V,
              I =
                              Ρ
                                     17mW,
                                                 1454.50hm
                    3.54mA,
                                             R
                                V =
     5.11V,
              I =
                    5.16mA,
                              Р
                                     26mW,
                                             R
                                                  990.10hm
                                =
V =
     5.12V,
              I =
                    9.43mA,
                                     49mW,
                                             R =
                                                  542.80hm
                                =
V =
                                             R =
                                                  382.70hm
     5.13V,
                   13.40mA,
                                     69mW,
                V =
     5.13V,
              Ι
                   16.16mA,
                              Р
                                     82mW,
                                             R
                                                  317.50hm
                V =
     5.08V,
                                             R
                                                  258.70hm
                   19.63mA,
                              Р
                                     98mW,
                V =
     5.05V,
                   24.76mA,
                                             R
                                                  204.00hm
                                    126mW,
                                V =
                                                  162.20hm
     5.07V,
                                             R
                   31.23mA,
                                    160mW,
                V =
     5.04V,
                   42.50mA,
                              Ρ
                                    216mW,
                                             R
                                                  118.60hm
                                V =
     4.38V,
                  110.48mA,
                                             R
                                                   39.60hm
              I =
                              Р
                                    446mW,
                                V =
     0.16V,
                  135.02mA,
                                     19mW,
                                             R
                                                    1.20hm
                                V =
     0.23V,
                  140.01mA,
                                             R
                                                    1.60hm
                              Р
                                     26mW,
                                V =
     0.13V,
              I =
                  144.61mA,
                                     15mW,
                                             R
                                                    0.90hm
                                V =
                  149.01mA,
     0.12V,
                                                    0.80hm
                                     18mW,
                                             R
```



How can we plot the result?

- Connect plotter to ESP32?
 - And run Matlab or Excel?
- Better solution
 - Do the plotting on a computer that's made for this (e.g. laptop)
 - How do we get the data there?

Summary

IoT Application

- Circuits
- Python
- Internet ...
- Sensors
 - INA219
 - I2C
 - Driver
- Prototyping
 - Wiring
 - Electrical and software testing